

QUESTIONS BEFORE STARTING THE QUESTION PAPER  
QUESTIONS ARE COMPULSORY.  
CANDIDATES MUST RETURN THE QUESTION PAPER SHEET TO THE INVIGILATOR CONCERNED BEFORE LEAVING THE EXAMINATION HALL, FAILING WHICH A CASE OF USE OF UNFAIR MEANS / MIS-BEHAVIOUR WILL BE REGISTERED AGAINST HIM / HER, IN ADDITION TO LODGING OF AN FIR WITH THE POLICE. FURTHER THE ANSWER SHEET OF SUCH A CANDIDATE WILL NOT BE EVALUATED.  
KEEPING IN VIEW THE TRANSPARENCY OF THE EXAMINATION SYSTEM, CARBONLESS OMR SHEET IS PROVIDED TO THE CANDIDATE SO THAT A COPY OF OMR SHEET MAY BE KEPT BY THE CANDIDATE.  
QUESTION BOOKLET ALONG WITH ANSWER KEY OF ALL THE A, B, C, D CODE WILL BE GOT UPLOADED ON THE UNIVERSITY WEBSITE AFTER THE CONDUCT OF ENTRANCE EXAMINATION. IN CASE THERE IS ANY DISCREPANCY IN THE QUESTION BOOKLET / ANSWER KEY, THE SAME MAY BE BROUGHT TO THE NOTICE OF THE CONTROLLER OF EXAMINATION IN WRITING THROUGH E.MAIL WITHIN 24 HOURS OF UPLOADING THE SAME ON THE UNIVERSITY WEBSITE. THEREAFTER, NO COMPLAINT IN ANY CASE, WILL BE CONSIDERED.  
THE CANDIDATE MUST NOT DO ANY ROUGH WORK OR WRITING IN THE OMR ANSWER SHEET. ROUGH WORK, IF ANY, MAY BE DONE IN THE QUESTION BOOK-LET ITSELF. ANSWERS MUST NOT BE TICKED IN THE QUESTION BOOK-LET.  
THERE WILL BE NO NEGATIVE MARKING. EACH CORRECT ANSWER WILL BE AWARDED ONE FULL MARK. CUTTING, ERASING, OVERWRITING AND MORE THAN ONE ANSWER IN OMR ANSWER SHEET WILL BE TREATED AS INCORRECT ANSWER.  
USE ONLY BLACK OR BLUE BALL POINT PEN OF GOOD QUALITY IN THE OMR ANSWER SHEET.  
BEFORE ANSWERING THE QUESTIONS, THE CANDIDATES SHOULD ENSURE THAT THEY HAVE BEEN SUPPLIED CORRECT AND COMPLETE BOOK-LET. COMPLAINTS, IF ANY, REGARDING MISPRINTING ETC. WILL NOT BE ENTERTAINED 30 MINUTES AFTER STARTING OF THE EXAMINATION.

(Set-“X”)

(DO NOT OPEN THIS QUESTION BOOKLET BEFORE TIME OR UNTIL YOU ARE ASKED TO DO SO)

(M.Phil/Ph.D/URS-EE-2018)

Code

**A**

Electronics & Communication  
Engineering

Sr. No. **100001**

Time : 1½ Hours

Max. Marks : 100

Total Questions : 100

Roll No. \_\_\_\_\_ (in figure) \_\_\_\_\_ (in words)

Name : \_\_\_\_\_ Father's Name : \_\_\_\_\_

Mother's Name : \_\_\_\_\_ Date of Examination : \_\_\_\_\_

(Signature of the candidate)



(Signature of the Invigilator)

**CANDIDATES MUST READ THE FOLLOWING INFORMATION/ INSTRUCTIONS BEFORE STARTING THE QUESTION PAPER.**

1. All questions are compulsory.
2. The candidates must return the Question book-let as well as OMR answer-sheet to the Invigilator concerned before leaving the Examination Hall, failing which a case of use of unfair-means / mis-behaviour will be registered against him / her, in addition to lodging of an FIR with the police. Further the answer-sheet of such a candidate will not be evaluated.
3. Keeping in view the transparency of the examination system, carbonless OMR Sheet is provided to the candidate so that a copy of OMR Sheet may be kept by the candidate.
4. Question Booklet along with answer key of all the A, B, C, D code will be got uploaded on the University website after the conduct of Entrance Examination. In case there is any discrepancy in the Question Booklet / Answer Key, the same may be brought to the notice of the Controller of Examination in writing / through E.Mail within 24 hours of uploading the same on the University Website. Thereafter, no complaint in any case, will be considered
5. The candidate MUST NOT do any rough work or writing in the OMR Answer-Sheet. Rough work, if any, may be done in the question book-let itself. Answers MUST NOT be ticked in the Question book-let.
6. There will be no Negative marking. Each correct answer will be awarded one full mark. Cutting, erasing, overwriting and more than one answer in OMR Answer-Sheet will be treated as incorrect answer.
7. Use only Black or Blue **BALL POINT PEN** of good quality in the OMR Answer-Sheet.
8. BEFORE ANSWERING THE QUESTIONS, THE CANDIDATES SHOULD ENSURE THAT THEY HAVE BEEN SUPPLIED CORRECT AND COMPLETE BOOK-LET. COMPLAINTS, IF ANY, REGARDING MISPRINTING ETC. WILL NOT BE ENTERTAINED 30 MINUTES AFTER STARTING OF THE EXAMINATION.

Confidential

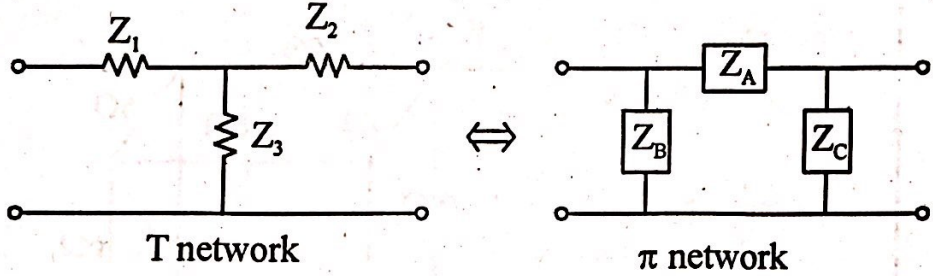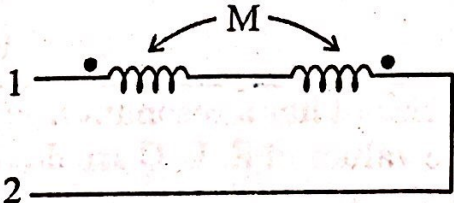

Question No.	Questions
1.	<p>T to <math>\pi</math> transformation gives the value of <math>Z_C \Rightarrow</math></p> <div style="text-align: center;">  <p>T network <span style="margin-left: 200px;">⇔</span> <span style="margin-left: 200px;">π network</span></p> </div> <p>(1) <math>Z_C = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_1}</math>      (2) <math>Z_C = \frac{Z_A Z_B}{Z_A + Z_B + Z_C}</math></p> <p>(3) <math>Z_C = \frac{Z_A + Z_B + Z_C}{Z_A Z_B + Z_A Z_C + Z_B Z_C}</math>      (4) <math>Z_C = \frac{Z_1 Z_2 Z_3}{Z_1 + Z_2 + Z_3}</math></p>
2.	<p>In the above question <math>\pi</math> to T conversion gives the value of <math>Z_1</math></p> <p>(1) <math>\frac{Z_B Z_C}{Z_A + Z_B + Z_C}</math>      (2) <math>\frac{Z_A + Z_B + Z_C}{Z_A Z_B + Z_B Z_C + Z_C Z_A}</math></p> <p>(3) <math>\frac{Z_1 + Z_2}{Z_1 + Z_2 + Z_3}</math>      (4) <math>\frac{Z_A Z_B}{Z_A + Z_B + Z_C}</math></p>
3.	<p>The equivalent inductance of the following is given by</p> <div style="text-align: center;">  </div> <p>(1) <math>L_1 + L_2 + M</math>      (2) <math>L_1 + L_2 - M</math></p> <p>(3) <math>L_1 + L_2 + 2M</math>      (4) <math>L_1 + L_2 - 2M</math></p>











Question No.	Questions
12.	<p>Fermi Level for a P-type semiconductor is given by</p> <p>(1) <math>E_F = E_V - KT \ln \frac{N_A}{N_V}</math>                      (2) <math>E_F = -E_V + KT \ln \frac{N_A}{N_V}</math></p> <p>(3) <math>E_F = E_V - K_T \ln \frac{N_A}{N_V}</math>                      (4) <math>E_F = E_C - K_T \ln \frac{N_C}{N_D}</math></p>
13.	<p>For conductors the value of Hall coefficient is given by</p> <p>(1) <math>R_H = \frac{1}{nq}</math>    (2) <math>R_H = \frac{nq}{\mu_n}</math></p> <p>(3) <math>R_H = \frac{\mu_p}{nq}</math>    (4) <math>R_H = \frac{n\mu_n + p\mu_p}{q}</math></p>
14.	<p>The band gap energy of Ge at 300 °K is given by</p> <p>(1) <math>E_g = 0.785 \text{ eV}</math>    (2) <math>E_g = 1.121 \text{ eV}</math></p> <p>(3) <math>E_g = 0.7181 \text{ eV}</math>    (4) <math>E_g = 1.212 \text{ eV}</math></p>
15.	<p>Under low level injection assumption, the injected minority current for an extrinsic semiconductor is essentially the</p> <p>(1) Diffusion current    (2) Drift current</p> <p>(3) Recombination current    (4) Induction current</p>
16.	<p>Ga As has band gap energy of the order of</p> <p>(1) 1.43 eV    (2) 0.7 eV</p> <p>(3) 2.4 eV    (4) 1.6 eV</p>
17.	<p>Typical value of impurity concentration in a tunnel diode is</p> <p>(1) 1 part in <math>10^8</math> parts    (2) 1 part in <math>10^3</math> parts</p> <p>(3) 1 PPM    (4) 1 part in 10 parts</p>







Question No.	Questions
23.	<p>If the source resistance, the output resistance of emitter follower using the simplified hybrid model would be</p> <p>(1) <math>\frac{h_{ie} + R_s}{1 + h_{fe}}</math>                      (2) <math>\frac{h_{ie} + R_s}{h_{fe}}</math></p> <p>(3) <math>R_s + \frac{1}{h_{oe}}</math>                      (4) <math>\frac{1}{h_{oe}}</math></p>
24.	<p>The ripple factor is given by</p> <p>(1) <math>\sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}</math>                      (2) <math>\left(1 - \sqrt{\frac{I_{rms}}{I_{dc}}}\right)^2</math></p> <p>(3) <math>\frac{I_{rms}}{I_{dc}}</math>                      (4) <math>\frac{I_{dc}}{I_{rms}}</math></p>
25.	<p>Following circuits is given by :</p> <div style="text-align: center;"> </div> <p>(1) Bridge rectifier                      (2) Ring modulator</p> <p>(3) Frequency discriminator                      (4) Voltage doubler.</p>
26.	<p>For a transistor amplifier to be inherently stable against thermal runaway, the condition is</p> <p>(1) <math>V_{CE} &gt; \frac{V_{CC}}{2}</math>                      (2) <math>V_{CE} &lt; \frac{V_{CC}}{2}</math></p> <p>(3) <math>V_{CE} = \frac{V_{CC}}{2}</math>                      (4) <math>V_{CE} = 1.5 V_{CC}</math></p>












Question No.	Questions
38.	<p>Which one of following is not a synchronous input with reference to a flip flop</p> <p>(1) J input in JK flip flop                      (2) R input in RS flip flop  (3) Preset input in JK flip flop                (4) D-input in a D flip flop</p>
39.	<p>A counter having a modulus of 64 should have a minimum of</p> <p>(1) Six flip flops                                      (2) Seven flip flops  (3) 5 - D - flip flops                                (4) 64 flip flops</p>
40.	<p>A logic circuit that gives a pulsed waveform at the output for a sinusoidal input</p> <p>(1) Bi stable multivibrator                      (2) Monostable multivibrator  (3) Astable multivibrator                         (4) Schmitt trigger</p>
41.	<p>Poisson's equation is given by</p> <p>(1) <math>\nabla \cdot D = 0</math>                                      (2) <math>\nabla^2 V = 0</math>  (3) <math>\nabla^2 V = -\frac{\rho}{\epsilon}</math>                                      (4) <math>\nabla^2 V = \frac{\rho}{\epsilon_0}</math></p>
42.	<p>The total flux of a closed surface is equal to the net charge enclosed within the surface. This statement is an expression of</p> <p>(1) Divergence Theorem                          (2) Gauss's Law  (3) Faraday Law                                      (4) Maxwells equations</p>
43.	<p>The divergence of a vector <math>\bar{A} = x \hat{a}_x + y \hat{a}_y + z \hat{a}_z</math> is</p> <p>(1) 0    (2) <math>\frac{1}{3}</math>  (3) 1    (4) 3</p>
44.	<p>Which of the following expression is true for a perfect dielectric</p> <p>(1) <math>\sigma \gg w\epsilon</math>                                      (2) <math>\sigma = w\epsilon</math>  (3) <math>\sigma \ll w\epsilon</math>                                      (4) <math>\sigma = \sqrt{w\epsilon}</math></p>





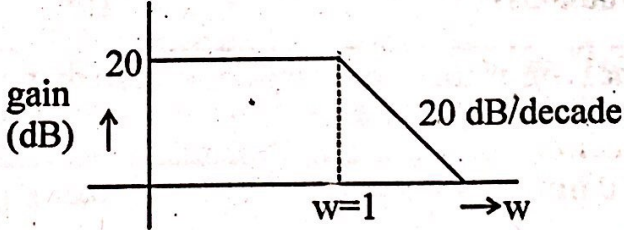

Question No.	Questions
51.	<p>The open loop transfer function of a certain control system is given by <math>GH = \frac{K}{(S+2)^3}</math> for <math>K &gt; 0</math>. For what value of gain factor, <math>K</math>, will the root locus of the control system cross the <math>jw</math>-axis.</p> <p>(1) 8 (2) 14 (3) 24 (4) 64</p>
52.	<p>For the above question, the value of the damping factor <math>\xi</math> for a design value of gain factor equal to 8 ?</p> <p>(1) 0.5 (2) 0.3 (3) 0.707 (4) 0.866</p>
53.	<p>A system has 14 poles and 2-zeros. Its high frequency asymptote in its magnitude plot will have a slope of</p> <p>(1) -40 dB/decade (2) -240 dB/decade (3) -280 dB/decade (4) -320 dB/decade</p>
54.	<p>Bode plot of a stable system is shown in the following figure. The transfer function of the system is :</p> <div style="text-align: center;">  <p>The figure shows a Bode magnitude plot. The vertical axis is labeled 'gain (dB)' with an upward arrow, and the horizontal axis is labeled 'w' with a rightward arrow. A horizontal line is drawn at a gain of 20 dB. A vertical dashed line drops from the end of this horizontal line to the horizontal axis at the point labeled 'w=1'. From this point, a line with a negative slope descends, labeled '20 dB/decade'.</p> </div> <p>(1) <math>\frac{1}{(S+1)}</math> (2) <math>\frac{10}{(S+1)}</math> (3) <math>\frac{1}{S(S+1)}</math> (4) <math>\frac{10}{s(s+1)}</math></p>















Question No.	Questions
73.	<p>For a bit rate of 8 kbps, the best possible values of the transmitted frequencies in a coherent binary FSK system are</p> <p>(1) 16 kHz and 20 kHz                      (2) 20 kHz and 32 kHz  (3) 20 kHz and 40 kHz                      (4) 32 kHz and 40 kHz</p>
74.	<p>Which function displays a string of text and append a new line character at its end ?</p> <p>(1) putchar ( )                      (2) printf ( )  (3) puts ( )                      (4) put ( )</p>
75.	<p>What will be output of the following code if <math>i = 10</math> and <math>a[10] = 20</math> ;  <math>a [i] = i ++</math> ;</p> <p>(1) <math>a [10]</math> will be 10                      (2) <math>a [11]</math> will be 11  (3) <math>a [11]</math> will be 10                      (4) None of the above</p>
76.	<p>Following statement is given</p> <pre>a = 0; b = (a = 0) ? 2 : 3;</pre> <p>What will be the value of b</p> <p>(1) 2                      (2) 3  (3) 0                      (4) 1</p>
77.	<p>Find the output for the following C program :</p> <pre>main ( ) {int x = 2, y = 6, z = 6;   x = y == z;   printf (" % d", x)</pre> <p>(1) 1                      (2) 2  (3) 6                      (4) 8</p>







Question No.	Questions
83.	<p>Normal probability curve is denoted by</p> <p>(1) <math>\frac{1}{\sigma\sqrt{2\pi}} \exp(x^2 / 2\sigma^2)</math>                      (2) <math>\frac{1}{\sigma\sqrt{2\pi}} e^{x/2\sigma^2}</math></p> <p>(3) <math>\frac{1}{\sigma\sqrt{2\pi}} \exp(-x^2 / 2\sigma^2)</math>                      (4) <math>\frac{1}{\sigma\sqrt{2\pi}} \exp(x^3 / 2\sigma^3)</math></p>
84.	<p>Relative static error may be defined as</p> <p>(1) <math>\frac{\text{true value}}{\text{Absolute Error}}</math>                      (2) <math>\frac{\text{true value} - \text{Absolute Error}}{\text{true value}}</math></p> <p>(3) <math>\frac{\text{Absolute Error}}{\text{true value} + \text{Absolute Error}}</math>                      (4) <math>\frac{\text{Absolute Error}}{\text{true value}}</math></p>
85.	<p>Static sensitivity at an operating point is given by</p> <p>(1) <math>\frac{\text{infinitesimal change in the output}}{\text{infinitesimal change in the input}}</math></p> <p>(2) <math>\frac{\text{infinitesimal change in the input}}{\text{infinitesimal change in the output}}</math></p> <p>(3) <math>\frac{\text{true value}}{\text{Absolute value}}</math></p> <p>(4) <math>\frac{\text{Absolute value}}{\text{true value}}</math></p>
86.	<p>The input impedance of a cathode ray oscilloscope is of the order of</p> <p>(1) 10 <math>\Omega</math>                      (2) Mega ohms</p> <p>(3) Kilo ohms                      (4) fraction of 1 ohms</p>











Question No.	Questions
98.	Class 'C' chopper works in the following quadrants (1) 1st (2) 2nd (3) 1st & 2nd (4) All quadrants
99.	Induction heating is used for (1) Volume heating (2) Plastic packing (3) Plyboard industry (4) Surface heating
100.	For speed control of ac motors following are used (1) Cyclo converters (2) Choppers (3) Rectifiers (4) UJT and SCR



(Set-“X”)

(DO NOT OPEN THIS QUESTION BOOKLET BEFORE TIME OR UNTIL YOU ARE ASKED TO DO SO)

(M.Phil/Ph.D/URS-EE-2018)

Electronics & Communication  
Engineering

Sr. No. **100022**

Code **B**

Time : 1¼ Hours

Max. Marks : 100

Total Questions : 100

Roll No. \_\_\_\_\_ (in figure) \_\_\_\_\_ (in words)

Name : \_\_\_\_\_ Father's Name : \_\_\_\_\_

Mother's Name : \_\_\_\_\_ Date of Examination : \_\_\_\_\_

(Signature of the candidate)

(Signature of the Invigilator)

**CANDIDATES MUST READ THE FOLLOWING INFORMATION/INSTRUCTIONS BEFORE STARTING THE QUESTION PAPER.**


1. All questions are compulsory.
2. The candidates must return the Question book-let as well as OMR answer-sheet to the Invigilator concerned before leaving the Examination Hall, failing which a case of use of unfair-means / mis-behaviour will be registered against him / her, in addition to lodging of an FIR with the police. Further the answer-sheet of such a candidate will not be evaluated.
3. Keeping in view the transparency of the examination system, carbonless OMR Sheet is provided to the candidate so that a copy of OMR Sheet may be kept by the candidate.
4. Question Booklet along with answer key of all the A, B, C, D code will be got uploaded on the University website after the conduct of Entrance Examination. In case there is any discrepancy in the Question Booklet / Answer Key, the same may be brought to the notice of the Controller of Examination in writing / through E.Mail within 24 hours of uploading the same on the University Website. Thereafter, no complaint in any case, will be considered
5. The candidate **MUST NOT** do any rough work or writing in the OMR Answer-Sheet. Rough work, if any, may be done in the question book-let itself. Answers **MUST NOT** be ticked in the Question book-let.
6. There will be no Negative marking. Each correct answer will be awarded one full mark. Cutting, erasing, overwriting and more than one answer in OMR Answer-Sheet will be treated as incorrect answer.
7. Use only Black or Blue **BALL POINT PEN** of good quality in the OMR Answer-Sheet.
8. **BEFORE ANSWERING THE QUESTIONS, THE CANDIDATES SHOULD ENSURE THAT THEY HAVE BEEN SUPPLIED CORRECT AND COMPLETE BOOK-LET. COMPLAINTS, IF ANY, REGARDING MISPRINTING ETC. WILL NOT BE ENTERTAINED 30 MINUTES AFTER STARTING OF THE EXAMINATION.**





Question No.	Questions
1.	<p>Current density in a semiconductor material is given by</p> <p>(1) <math>J = n \mu_n q/E</math> (2) <math>J = p \mu_p q/E</math>  (3) <math>J = (n \mu_n + p \mu_p) \cdot E</math> (4) <math>J = (n \mu_n + p \mu_p) / E</math></p>
2.	<p>Fermi Level for a P-type semiconductor is given by</p> <p>(1) <math>E_F = E_V - KT \ln \frac{N_A}{N_V}</math> (2) <math>E_F = -E_V + KT \ln \frac{N_A}{N_V}</math>  (3) <math>E_F = E_V - K_T \ln \frac{N_A}{N_V}</math> (4) <math>E_F = E_C - K_T \ln \frac{N_C}{N_D}</math></p>
3.	<p>For conductors the value of Hall coefficient is given by</p> <p>(1) <math>R_H = \frac{1}{nq}</math> (2) <math>R_H = \frac{nq}{\mu_n}</math>  (3) <math>R_H = \frac{\mu_p}{nq}</math> (4) <math>R_H = \frac{n\mu_n + p\mu_p}{q}</math></p>
4.	<p>The band gap energy of Ge at 300 K is given by</p> <p>(1) <math>E_g = 0.785 \text{ eV}</math> (2) <math>E_g = 1.121 \text{ eV}</math>  (3) <math>E_g = 0.7181 \text{ eV}</math> (4) <math>E_g = 1.212 \text{ eV}</math></p>
5.	<p>Under low level injection assumption, the injected minority current for an extrinsic semiconductor is essentially the</p> <p>(1) Diffusion current (2) Drift current  (3) Recombination current (4) Induction current</p>
6.	<p>Ga As has band gap energy of the order of</p> <p>(1) 1.43 eV (2) 0.7 eV  (3) 2.4 eV (4) 1.6 eV</p>

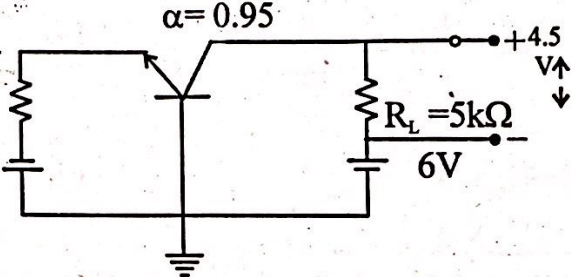

Question No.	Questions
7.	Typical value of impurity concentration in a tunnel diode is (1) 1 part in $10^8$ parts                      (2) 1 part in $10^3$ parts (3) 1 PPM    (4) 1 part in 10 parts
8.	In the given circuit, the value of collector current is :  (1) 0.8 mA    (2) 0.9 mA (3) 0.947 mA                                        (4) 0.847 A
9.	MOSFET can be used as a (1) Current controlled capacitor              (2) Voltage controlled capacitor (3) Current controlled inductor              (4) Voltage controlled inductor
10.	The effective channel length of a MOSFET in saturation decreases with the increase in (1) Gate voltage                                      (2) Drain voltage (3) Source voltage                                    (4) Body voltage
11.	8086 has basic no. of instructions (1) 64    (2) 117 (3) 128    (4) 256
12.	The starting address of an interrupt is called (in 8086 Micro processor) (1) stack pointer                                      (2) program counter (3) interrupt output                                    (4) interrupt vector








Question No.	Questions
18.	Class 'C' chopper works in the following quadrants (1) 1st (2) 2nd (3) 1st & 2nd (4) All quadrants
19.	Induction heating is used for (1) Volume heating (2) Plastic packing (3) Plyboard industry (4) Surface heating
20.	For speed control of ac motors following are used (1) Cyclo converters (2) Choppers (3) Rectifiers (4) UJT and SCR
21.	The Nyquist rate for message signal given by $m(t) = 10 \cos 10^3 \pi t \cdot \cos 4 \times 10^3 \pi t$ is (1) 10 kHz (2) 2.5 kHz (3) 5 kHz (4) 2 kHz
22.	Compression in PCM refers to relative compression of (1) Lower signal amplitudes (2) Higher signal amplitudes (3) Lower signal frequencies (4) Higher signal frequencies
23.	For a bit rate of 8 kbps, the best possible values of the transmitted frequencies in a coherent binary FSK system are (1) 16 kHz and 20 kHz (2) 20 kHz and 32 kHz (3) 20 kHz and 40 kHz (4) 32 kHz and 40 kHz
24.	Which function displays a string of text and append a new line character at its end ? (1) putchar ( ) (2) printf ( ) (3) puts ( ) (4) put ( )
25.	What will be output of the following code if $i = 10$ and $a[10] = 20$ $a[i] = i++;$ (1) $a[10]$ will be 10 (2) $a[11]$ will be 11 (3) $a[11]$ will be 10 (4) None of the above





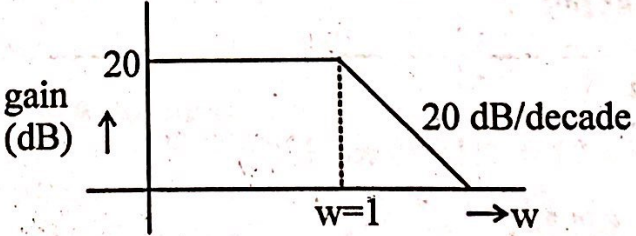

Question No.	Questions
30.	FORTRAN is a (1) High level language                      (2) Low level language (3) OOP language                              (4) Machine language
31.	The open loop transfer function of a certain control system is given by $GH = \frac{K}{(S+2)^3}$ for $K > 0$ . For what value of gain factor, $K$ , will the root locus of the control system cross the $j\omega$ -axis. (1) 8    (2) 14 (3) 24    (4) 64
32.	For the above question, the value of the damping factor $\xi$ for a design value of gain factor equal to 8 ? (1) 0.5    (2) 0.3 (3) 0.707    (4) 0.866
33.	A system has 14 poles and 2-zeroes. Its high frequency asymptote in its magnitude plot will have a slope of (1) -40 dB/decade                                      (2) -240 dB/decade (3) -280 dB/decade                                    (4) -320 dB/decade
34.	Bode plot of a stable system is shown in the following figure. The transfer function of the system is : <div style="text-align: center;">  <p>The figure shows a Bode magnitude plot. The vertical axis is labeled 'gain (dB)' with an upward arrow. The horizontal axis is labeled 'w' with a rightward arrow. A horizontal line is drawn at 20 dB. A vertical dashed line is drawn at w=1. From the point (1, 20), a line with a negative slope of 20 dB/decade extends downwards and to the right.</p> </div> (1) $\frac{1}{(S+1)}$ (2) $\frac{10}{(S+1)}$ (3) $\frac{1}{S(S+1)}$ (4) $\frac{10}{s(s+1)}$







Question No.	Questions
41.	The octal equivalent of Hexadecimal number 2E.C1 would be (1) 212.602 (2) 56.602 (3) 56.623 (4) 65.302
42.	The complement of complement of $\bar{A}B + A\bar{B}$ will be (1) $AB + \bar{A}\bar{B}$ (2) $\bar{A}B$ (3) $\bar{A}B + A\bar{B}$ (4) $\bar{A}B \cdot (\bar{A} + B)$
43.	What is minimum number of 2-input NAND gates required to complement a 2-input OR gate (1) 2 (2) 4 (3) 3 (4) 5
44.	A basic CMOS two input NAND gate requires (1) Two N-channel MOSFETs (2) Two N-Channel & two P-channel MOSFETs (3) Two P-Channel MOSFETs (4) One N-Channel and one P-channel MOSFET
45.	IC 7402 is a - 2 input (1) NAND gate (2) EX-OR gate (3) NOR gate (4) OR Gate
46.	A decoder is nothing but a DEMUX without (1) control inputs (2) data input (3) enable input (4) clock
47.	The size of a PROM needed to implement a dual 8 to 1 MUX with common selection inputs would be (1) 256 K × 2 (2) 512 K × 2 (3) 1024 K × 2 (4) 128 K × 2
48.	Which one of following is not a synchronous input with reference to a flip flop (1) J input in JK flip flop (2) R input in RS flip flop (3) Preset input in JK flip flop (4) D-input in a D flip flop



Question No.	Questions
49.	<p>A counter having a modulus of 64 should have a minimum of</p> <p>(1) Six flip flops (2) Seven flip flops (3) 5 – D – flip flops (4) 64 flip flops</p>
50.	<p>A logic circuit that gives a pulsed waveform at the output for a sinusoidal input</p> <p>(1) Bi stable multivibrator (2) Monostable multivibrator (3) Astable multivibrator (4) Schmitt trigger</p>
51.	<p>For a common base BJT, having <math>I_e = 5 \text{ mA}</math> and <math>\alpha = 0.97</math> an AC signal of 5 mV is applied between the base and the emitter terminals. The input impedance is given by</p> <p>(1) <math>5.2 \Omega</math> (2) <math>6 \Omega</math> (3) <math>4.9 \Omega</math> (4) <math>6.7 \Omega</math></p>
52.	<p>The typical value of <math>h_f</math> for common base BJT is</p> <p>(1) 50 – 250 (2) – 50 (3) – 1 (4) 25</p>
53.	<p>If the source resistance, the output resistance of emitter follower using the simplified hybrid model would be</p> <p>(1) <math>\frac{h_{ie} + R_s}{1 + h_{fe}}</math> (2) <math>\frac{h_{ie} + R_s}{h_{fe}}</math> (3) <math>R_s + \frac{1}{h_{oe}}</math> (4) <math>\frac{1}{h_{oe}}</math></p>
54.	<p>The ripple factor is given by</p> <p>(1) <math>\sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2} - 1</math> (2) <math>\left(1 - \sqrt{\frac{I_{rms}}{I_{dc}}}\right)^2</math> (3) <math>\frac{I_{rms}}{I_{dc}}</math> (4) <math>\frac{I_{dc}}{I_{rms}}</math></p>























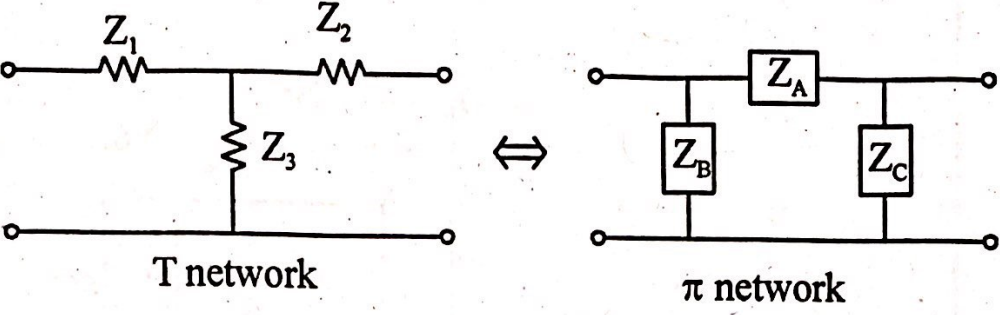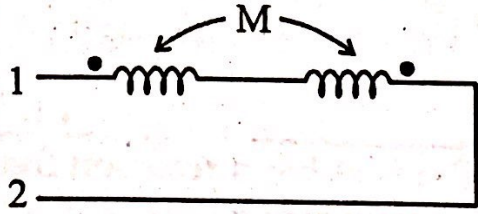

Question No.	Questions
81.	<p>T to <math>\pi</math> transformation gives the value of <math>Z_C \Rightarrow</math></p> <div style="display: flex; justify-content: center; align-items: center;">  </div> <p>(1) <math>Z_C = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_1}</math>      (2) <math>Z_C = \frac{Z_A Z_B}{Z_A + Z_B + Z_C}</math></p> <p>(3) <math>Z_C = \frac{Z_A + Z_B + Z_C}{Z_A Z_B + Z_A Z_C + Z_B Z_C}</math>      (4) <math>Z_C = \frac{Z_1 Z_2 Z_3}{Z_1 + Z_2 + Z_3}</math></p>
82.	<p>In the above question <math>\pi</math> to T conversion gives the value of <math>Z_1</math></p> <p>(1) <math>\frac{Z_B Z_C}{Z_A + Z_B + Z_C}</math>      (2) <math>\frac{Z_A + Z_B + Z_C}{Z_A Z_B + Z_B Z_C + Z_C Z_A}</math></p> <p>(3) <math>\frac{Z_1 + Z_2}{Z_1 + Z_2 + Z_3}</math>      (4) <math>\frac{Z_A Z_B}{Z_A + Z_B + Z_C}</math></p>
83.	<p>The equivalent inductance of the following is given by</p> <div style="text-align: center;">  </div> <p>(1) <math>L_1 + L_2 + M</math>      (2) <math>L_1 + L_2 - M</math></p> <p>(3) <math>L_1 + L_2 + 2M</math>      (4) <math>L_1 + L_2 - 2M</math></p>











Question No.	Questions
91.	<p>Three resistances <math>R_1 = 37 \text{ ohm} \pm 5\%</math>, <math>R_2 = 75 \text{ ohm} \pm 5\%</math>, <math>R_3 = 50 \text{ ohm} \pm 5\%</math>, Determine the value of series resistance error if they are connected in series</p> <p>(1) <math>\pm 5\%</math> (2) <math>\pm 7.5\%</math>  (3) <math>\pm 3.5\%</math> (4) <math>\pm 8.10\%</math></p>
92.	<p>A <math>160 \pm 0\%</math> PF capacitor, an inductor of <math>160 \mu\text{H}</math> and a resistor of <math>1200 \pm 10 \Omega</math> are connected in series. The value of resonant frequency is</p> <p>(1) 1000 kHz (2) 100 kHz  (3) 1.1 MHz (4) 0.9 MHz</p>
93.	<p>Normal probability curve is denoted by</p> <p>(1) <math>\frac{1}{\sigma\sqrt{2\pi}} \exp(x^2/2\sigma^2)</math> (2) <math>\frac{1}{\sigma\sqrt{2\pi}} e^{x/2\sigma^2}</math>  (3) <math>\frac{1}{\sigma\sqrt{2\pi}} \exp(-x^2/2\sigma^2)</math> (4) <math>\frac{1}{\sigma\sqrt{2\pi}} \exp(x^3/2\sigma^3)</math></p>
94.	<p>Relative static error may be defined as</p> <p>(1) <math>\frac{\text{true value}}{\text{Absolute Error}}</math> (2) <math>\frac{\text{true value} - \text{Absolute Error}}{\text{true value}}</math>  (3) <math>\frac{\text{Absolute Error}}{\text{true value} + \text{Absolute Error}}</math> (4) <math>\frac{\text{Absolute Error}}{\text{true value}}</math></p>







Question No.	Questions	Question No.
98.	<p>The transfer function of a system is <math>G(s) = \frac{100e^{-st}}{s(s+10)}</math>, the system</p> <p>(1) is a linear system                      (2) is a nonlinear system</p> <p>(3) has a transportation lag              (4) None of the above</p>	98.
99.	<p>8086 microprocessor has address bus of</p> <p>(1) 16 bits                                      (2) 24 bits</p> <p>(3) 20 bits                                      (4) 8 bits</p>	99.
100.	<p>8086 has a bus cycle of at least</p> <p>(1) 4 clock periods                      (2) 2 clock periods</p> <p>(3) 3 clock periods                      (4) None of these</p>	100.
	<p>Mega ohms                                      (1) 10 Ω</p> <p>fraction of 1 ohms                              (2) Kilo ohms</p>	96.
	<p>The mean deviation <math>\bar{D}</math> in terms of deviations from the mean value of <math>n</math> readings is</p> <p>(1) <math>\frac{\sum  d }{n}</math></p> <p>(2) <math>\frac{\sum d^2}{n}</math></p> <p>(3) <math>\frac{\sum d}{n}</math></p> <p>(4) <math>\frac{\sum d^3}{n}</math></p>	97.



(Set-“X”)

(DO NOT OPEN THIS QUESTION BOOKLET BEFORE TIME OR UNTIL YOU ARE ASKED TO DO SO)

(M.Phil/Ph.D/URS-EE-2018)

Code

**C**

Electronics & Communication  
Engineering

Sr. No. **100003**

Time : 1¼ Hours

Max. Marks : 100

Total Questions : 100

Roll No. \_\_\_\_\_ (in figure) \_\_\_\_\_ (in words)

Name : \_\_\_\_\_ Father's Name : \_\_\_\_\_

Mother's Name : \_\_\_\_\_ Date of Examination : \_\_\_\_\_

(Signature of the candidate)

(Signature of the Invigilator)

**CANDIDATES MUST READ THE FOLLOWING INFORMATION/ INSTRUCTIONS BEFORE STARTING THE QUESTION PAPER.**

1. All questions are compulsory.
2. The candidates must return the Question book-let as well as OMR answer-sheet to the Invigilator concerned before leaving the Examination Hall, failing which a case of use of unfair-means / mis-behaviour will be registered against him / her, in addition to lodging of an FIR with the police. Further the answer-sheet of such a candidate will not be evaluated.
3. Keeping in view the transparency of the examination system, carbonless OMR Sheet is provided to the candidate so that a copy of OMR Sheet may be kept by the candidate.
4. Question Booklet along with answer key of all the A, B, C, D code will be got uploaded on the University website after the conduct of Entrance Examination. In case there is any discrepancy in the Question Booklet / Answer Key, the same may be brought to the notice of the Controller of Examination in writing / through E.Mail within 24 hours of uploading the same on the University Website. Thereafter, no complaint in any case, will be considered
5. The candidate **MUST NOT** do any rough work or writing in the OMR Answer-Sheet. Rough work, if any, may be done in the question book-let itself. Answers **MUST NOT** be ticked in the Question book-let.
6. **There will be no Negative marking. Each correct answer will be awarded one full mark. Cutting, erasing, overwriting and more than one answer in OMR Answer-Sheet will be treated as incorrect answer.**
7. Use only Black or Blue **BALL POINT PEN** of good quality in the OMR Answer-Sheet.
8. **BEFORE ANSWERING THE QUESTIONS, THE CANDIDATES SHOULD ENSURE THAT THEY HAVE BEEN SUPPLIED CORRECT AND COMPLETE BOOK-LET. COMPLAINTS, IF ANY, REGARDING MISPRINTING ETC. WILL NOT BE ENTERTAINED 30 MINUTES AFTER STARTING OF THE EXAMINATION.**




Question No.	Questions
1.	Poisson's equation is given by (1) $\nabla \cdot D = 0$ (2) $\nabla^2 V = 0$ (3) $\nabla^2 V = -\frac{\rho}{\epsilon}$ (4) $\nabla^2 V = \frac{\rho}{\epsilon_0}$
2.	The total flux of a closed surface is equal to the net charge enclosed within the surface. This statement is an expression of (1) Divergence Theorem (2) Gauss's Law (3) Faraday Law (4) Maxwells equations
3.	The divergence of a vector $\bar{A} = x \hat{a}_x + y \hat{a}_y + z \hat{a}_z$ is (1) 0 (2) $\frac{1}{3}$ (3) 1 (4) 3
4.	Which of the following expression is true for a perfect dielectric (1) $\sigma \gg w\epsilon$ (2) $\sigma = w\epsilon$ (3) $\sigma \ll w\epsilon$ (4) $\sigma = \sqrt{w\epsilon}$
5.	Given that $\sigma = 38 \text{ m S/m}$ & $\mu_r = 1$ for aluminium, the skin depth at a frequency of 2 MHz would be equal to (1) 64.5 nm (2) 64.5 $\mu\text{m}$ (3) 57.7 nm (4) 57.77 $\mu\text{m}$
6.	The power density of solar radiation at a place is $1.2 \text{ kW/m}^2$ . The approximate value of electric field corresponding to the incident solar power is given by (1) 950 V/m (2) 750 V/m (3) 450 V/m (4) 475 V/m






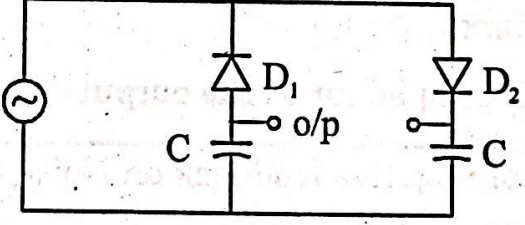


Question No.	Questions
13.	<p>If the source resistance, the output resistance of emitter follower using the simplified hybrid model would be</p> <p>(1) <math>\frac{h_{ie} + R_s}{1 + h_{fe}}</math>                      (2) <math>\frac{h_{ie} + R_s}{h_{fe}}</math></p> <p>(3) <math>R_s + \frac{1}{h_{oe}}</math>                      (4) <math>\frac{1}{h_{oe}}</math></p>
14.	<p>The ripple factor is given by</p> <p>(1) <math>\sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}</math>                      (2) <math>\left(1 - \sqrt{\frac{I_{rms}}{I_d}}\right)^2</math></p> <p>(3) <math>\frac{I_{rms}}{I_{dc}}</math>                      (4) <math>\frac{I_{dc}}{I_{rms}}</math></p>
15.	<p>Following circuits is given by :</p> <div style="text-align: center;">  </div> <p>(1) Bridge rectifier                      (2) Ring modulator</p> <p>(3) Frequency discriminator                      (4) Voltage doubler</p>
16.	<p>For a transistor amplifier to be inherently stable against thermal run away, the condition is</p> <p>(1) <math>V_{CE} &gt; \frac{V_{CC}}{2}</math>                      (2) <math>V_{CE} &lt; \frac{V_{CC}}{2}</math></p> <p>(3) <math>V_{CE} = \frac{V_{CC}}{2}</math>                      (4) <math>V_{CE} = 1.5 V_{CC}</math></p>





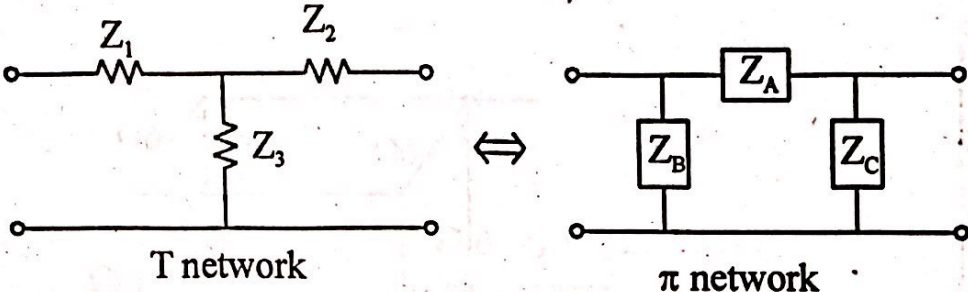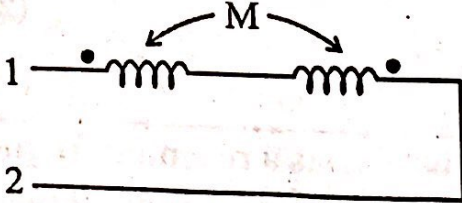


Question No.	Questions
21.	<p>T to <math>\pi</math> transformation gives the value of <math>Z_C \Rightarrow</math></p> <div style="display: flex; justify-content: center; align-items: center;">  </div> <p style="text-align: center;">T network <span style="margin-left: 200px;">π network</span></p> <p>(1) <math>Z_C = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_1}</math>      (2) <math>Z_C = \frac{Z_A Z_B}{Z_A + Z_B + Z_C}</math></p> <p>(3) <math>Z_C = \frac{Z_A + Z_B + Z_C}{Z_A Z_B + Z_A Z_C + Z_B Z_C}</math>      (4) <math>Z_C = \frac{Z_1 Z_2 Z_3}{Z_1 + Z_2 + Z_3}</math></p>
22.	<p>In the above question <math>\pi</math> to T conversion gives the value of <math>Z_1</math></p> <p>(1) <math>\frac{Z_B Z_C}{Z_A + Z_B + Z_C}</math>      (2) <math>\frac{Z_A + Z_B + Z_C}{Z_A Z_B + Z_B Z_C + Z_C Z_A}</math></p> <p>(3) <math>\frac{Z_1 + Z_2}{Z_1 + Z_2 + Z_3}</math>      (4) <math>\frac{Z_A Z_B}{Z_A + Z_B + Z_C}</math></p>
23.	<p>The equivalent inductance of the following is given by</p> <div style="text-align: center;">  </div> <p>(1) <math>L_1 + L_2 + M</math>      (2) <math>L_1 + L_2 - M</math></p> <p>(3) <math>L_1 + L_2 + 2M</math>      (4) <math>L_1 + L_2 - 2M</math></p>





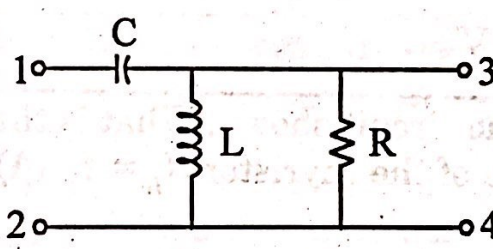

Question No.	Questions
27.	<p>In a series RLC circuit <math>R = 2k\Omega</math>, <math>L = 1H</math>, <math>C = \frac{1}{400} \mu F</math>, The resonant frequency is</p> <p>(1) <math>2 \times 10^4</math> Hz                      (2) <math>\frac{10^4}{\pi}</math> Hz</p> <p>(3) 10 kHz                                  (4) <math>20\pi</math> kHz</p>
28.	<p>For a 2-port network to be reciprocal, following is true</p> <p>(1) <math>Z_{11} = Z_{22}</math> and <math>Y_{11} = Y_{22}</math>                      (2) <math>Y_{21} = Y_{12}</math> &amp; <math>h_{21} = -h_{12}</math></p> <p>(3) <math>AD - BC = 0</math>                                  (4) <math>AB - CD = 0</math></p>
29.	<p>The network shown behaves like a</p> <div style="text-align: center;">  </div> <p>(1) High pass filter                                  (2) LPF</p> <p>(3) BPF    (4) Band stop filter</p>
30.	<p>If the scattering matrix <math>[S]</math> of a two port network is</p> $[S] = \begin{bmatrix} 0.2 \angle 0^\circ & 0.9 \angle 90^\circ \\ 0.9 \angle 90^\circ & 0.1 \angle 90^\circ \end{bmatrix}$ <p>then the network is</p> <p>(1) lossless and reciprocal                      (2) lossless but non reciprocal</p> <p>(3) lossy but reciprocal                                  (4) neither lossy nor reciprocal</p>
31.	<p>8086 has basic no. of instructions</p> <p>(1) 64    (2) 117</p> <p>(3) 128    (4) 256</p>







Question No.	Questions
37.	Chopper is used for conversion of (1) ac to dc (2) dc to ac (3) ac to ac (4) dc to dc
38.	Class 'C' chopper works in the following quadrants (1) 1st (2) 2nd (3) 1st & 2nd (4) All quadrants
39.	Induction heating is used for (1) Volume heating (2) Plastic packing (3) Plyboard industry (4) Surface heating
40.	For speed control of ac motors following are used (1) Cyclo converters (2) Choppers (3) Rectifiers (4) UJT and SCR
41.	The region of convergence of z-transform of the sequence $\left[\frac{5}{6}\right]^n u(n) - \left[\frac{6}{5}\right]^n u(-n-1)$ is (1) $ z  < \frac{5}{6}$ (2) $ z  > \frac{5}{6}$ (3) $\frac{5}{6} <  z  < \frac{6}{5}$ (4) $\frac{6}{5} <  z  < \infty$
42.	The power saving in case of SSB/SC signal as compared to a standard AM signal for modulation index = 0.5 is (1) 94.4% (2) 23.2% (3) 56.7% (4) 75%







Question No.	Questions
49.	<p>The input to a coherent detector is DSBSC signal plus Noise, the noise at the detector output is given by</p> <p>(1) In phase component                      (2) Quadrature component (3) Zero    (4) Envelope</p>
50.	<p>A Hilbert transformer is a</p> <p>(1) Non linear system                      (2) Non-causal system (3) Time-varying system                      (4) Low pass system</p>
51.	<p>The octal equivalent of Hexadecimal number 2E.C1 would be</p> <p>(1) 212.602                                      (2) 56.602 (3) 56.623                                      (4) 65.302</p>
52.	<p>The complement of complement of <math>\overline{A}B + A\overline{B}</math> will be</p> <p>(1) <math>AB + \overline{A}\overline{B}</math>                                      (2) <math>\overline{A}B</math> (3) <math>\overline{A}B + A\overline{B}</math>                                      (4) <math>\overline{A}B \cdot (\overline{A} + B)</math></p>
53.	<p>What is minimum number of 2-input NAND gates required to complement a 2-input OR gate</p> <p>(1) 2    (2) 4 (3) 3    (4) 5</p>
54.	<p>A basic CMOS two input NAND gate requires</p> <p>(1) Two N-channel MOSFETs (2) Two N-Channel &amp; two P-channel MOSFETs (3) Two P-Channel MOSFETs (4) One N-Channel and one P-channel MOSFET</p>
55.	<p>IC 7402 is a – 2 input,</p> <p>(1) NAND gate                                      (2) EX-OR gate (3) NOR gate                                      (4) OR Gate</p>







Question No.	Questions
63.	<p>For a bit rate of 8 kbps, the best possible values of the transmitted frequencies in a coherent binary FSK system are</p> <p>(1) 16 kHz and 20 kHz                      (2) 20 kHz and 32 kHz  (3) 20 kHz and 40 kHz                      (4) 32 kHz and 40 kHz</p>
64.	<p>Which function displays a string of text and append a new line character at its end ?</p> <p>(1) putchar ( )                                      (2) printf ( )  (3) puts ( )    (4) put ( )</p>
65.	<p>What will be output of the following code if <math>i = 10</math> and <math>a[10] = 20</math> ;  <math>a [i] = i ++</math> ;</p> <p>(1) <math>a [10]</math> will be 10                              (2) <math>a [11]</math> will be 11  (3) <math>a [11]</math> will be 10                              (4) None of the above</p>
66.	<p>Following statement is given</p> <pre>a = 0; b = (a = 0) ? 2 : 3;</pre> <p>What will be the value of b</p> <p>(1) 2    (2) 3  (3) 0    (4) 1</p>
67.	<p>Find the output for the following C program :</p> <pre>main ( ) {int x = 2, y = 6, z = 6;   x = y == z ;   printf (" % d", x)</pre> <p>(1) 1    (2) 2  (3) 6    (4) 8</p>







Question No.	Questions
73.	<p>Normal probability curve is denoted by</p> <p>(1) <math>\frac{1}{\sigma\sqrt{2\pi}} \exp(x^2 / 2\sigma^2)</math>                      (2) <math>\frac{1}{\sigma\sqrt{2\pi}} e^{x^2/2\sigma^2}</math></p> <p>(3) <math>\frac{1}{\sigma\sqrt{2\pi}} \exp(-x^2 / 2\sigma^2)</math>                      (4) <math>\frac{1}{\sigma\sqrt{2\pi}} \exp(x^3 / 2\sigma^3)</math></p>
74.	<p>Relative static error may be defined as</p> <p>(1) <math>\frac{\text{true value}}{\text{Absolute Error}}</math>                      (2) <math>\frac{\text{true value} - \text{Absolute Error}}{\text{true value}}</math></p> <p>(3) <math>\frac{\text{Absolute Error}}{\text{true value} + \text{Absolute Error}}</math>                      (4) <math>\frac{\text{Absolute Error}}{\text{true value}}</math></p>
75.	<p>Static sensitivity at an operating point is given by</p> <p>(1) <math>\frac{\text{infinitesimal change in the output}}{\text{infinitesimal change in the input}}</math></p> <p>(2) <math>\frac{\text{infinitesimal change in the input}}{\text{infinitesimal change in the output}}</math></p> <p>(3) <math>\frac{\text{true value}}{\text{Absolute value}}</math></p> <p>(4) <math>\frac{\text{Absolute value}}{\text{true value}}</math></p>
76.	<p>The input impedance of a cathode ray oscilloscope is of the order of</p> <p>(1) 10 <math>\Omega</math>                      (2) Mega ohms</p> <p>(3) Kilo ohms                      (4) fraction of 1 ohms</p>







Question No.	Questions
82.	<p>Fermi Level for a P-type semiconductor is given by</p> <p>(1) <math>E_F = E_V - KT \ln \frac{N_A}{N_V}</math>                      (2) <math>E_F = -E_V + KT \ln \frac{N_A}{N_V}</math></p> <p>(3) <math>E_F = E_V - K_T \ln \frac{N_A}{N_V}</math>                      (4) <math>E_F = E_C - K_T \ln \frac{N_C}{N_D}</math></p>
83.	<p>For conductors the value of Hall coefficient is given by</p> <p>(1) <math>R_H = \frac{1}{nq}</math>                                      (2) <math>R_H = \frac{nq}{\mu_n}</math></p> <p>(3) <math>R_H = \frac{\mu_p}{nq}</math>                                      (4) <math>R_H = \frac{n\mu_n + p\mu_p}{q}</math></p>
84.	<p>The band gap energy of Ge at 300 K is given by</p> <p>(1) <math>E_g = 0.785 \text{ eV}</math>                              (2) <math>E_g = 1.121 \text{ eV}</math></p> <p>(3) <math>E_g = 0.7181 \text{ eV}</math>                              (4) <math>E_g = 1.212 \text{ eV}</math></p>
85.	<p>Under low level injection assumption, the injected minority current for an extrinsic semiconductor is essentially the</p> <p>(1) Diffusion current                              (2) Drift current</p> <p>(3) Recombination current                      (4) Induction current</p>
86.	<p>Ga As has band gap energy of the order of</p> <p>(1) 1.43 eV    (2) 0.7 eV</p> <p>(3) 2.4 eV    (4) 1.6 eV</p>
87.	<p>Typical value of impurity concentration in a tunnel diode is</p> <p>(1) 1 part in <math>10^8</math> parts                              (2) 1 part in <math>10^3</math> parts</p> <p>(3) 1 PPM    (4) 1 part in 10 parts</p>















(Set-“X”)

(DO NOT OPEN THIS QUESTION BOOKLET BEFORE TIME OR UNTIL YOU ARE ASKED TO DO SO)

(M.Phil/Ph.D/URS-EE-2018)

Code

**D**

Electronics & Communication  
Engineering

Sr. No. **100004**

Time : 1¼ Hours

Max. Marks : 100

Total Questions : 100

Roll No. \_\_\_\_\_ (in figure) \_\_\_\_\_ (in words)

Name : \_\_\_\_\_ Father's Name : \_\_\_\_\_

Mother's Name : \_\_\_\_\_ Date of Examination : \_\_\_\_\_

(Signature of the candidate)

(Signature of the Invigilator)

**CANDIDATES MUST READ THE FOLLOWING INFORMATION/  
INSTRUCTIONS BEFORE STARTING THE QUESTION PAPER.**

1. All questions are compulsory.
2. The candidates must return the Question book-let as well as OMR answer-sheet to the Invigilator concerned before leaving the Examination Hall, failing which a case of use of unfair-means / mis-behaviour will be registered against him / her, in addition to lodging of an FIR with the police. Further the answer-sheet of such a candidate will not be evaluated.
3. Keeping in view the transparency of the examination system, carbonless OMR Sheet is provided to the candidate so that a copy of OMR Sheet may be kept by the candidate.
4. Question Booklet along with answer key of all the A, B, C, D code will be got uploaded on the University website after the conduct of Entrance Examination. In case there is any discrepancy in the Question Booklet / Answer Key, the same may be brought to the notice of the Controller of Examination in writing / through E.Mail within 24 hours of uploading the same on the University Website. Thereafter, no complaint in any case, will be considered
5. The candidate MUST NOT do any rough work or writing in the OMR Answer-Sheet. Rough work, if any, may be done in the question book-let itself. Answers MUST NOT be ticked in the Question book-let.
6. There will be no Negative marking. Each correct answer will be awarded one full mark. Cutting, erasing, overwriting and more than one answer in OMR Answer-Sheet will be treated as incorrect answer.
7. Use only Black or Blue **BALL POINT PEN** of good quality in the OMR Answer-Sheet.
8. BEFORE ANSWERING THE QUESTIONS, THE CANDIDATES SHOULD ENSURE THAT THEY HAVE BEEN SUPPLIED CORRECT AND COMPLETE BOOK-LET. COMPLAINTS, IF ANY, REGARDING MISPRINTING ETC. WILL NOT BE ENTERTAINED 30 MINUTES AFTER STARTING OF THE EXAMINATION.










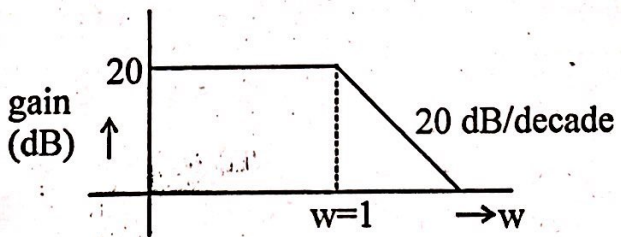

Question No.	Questions
11.	<p>The open loop transfer function of a certain control system is given by <math>GH = \frac{K}{(S+2)^3}</math> for <math>K &gt; 0</math>. For what value of gain factor, <math>K</math>, will the root locus of the control system cross the <math>jw</math>-axis.</p> <p>(1) 8 (2) 14 (3) 24 (4) 64</p>
12.	<p>For the above question, the value of the damping factor <math>\xi</math> for a design value of gain factor equal to 8 ?</p> <p>(1) 0.5 (2) 0.3 (3) 0.707 (4) 0.866</p>
13.	<p>A system has 14 poles and 2-zeroes. Its high frequency asymptote in its magnitude plot will have a slope of</p> <p>(1) -40 dB/decade (2) -240 dB/decade (3) -280 dB/decade (4) -320 dB/decade</p>
14.	<p>Bode plot of a stable system is shown in the following figure. The transfer function of the system is :</p> <div style="text-align: center;">  <p>The figure is a Bode magnitude plot. The vertical axis is labeled 'gain (dB)' with an upward arrow. The horizontal axis is labeled 'w' with a rightward arrow. The plot shows a horizontal line at 20 dB from the origin to a vertical dashed line at w=1. From w=1, the plot slopes downward at a rate of 20 dB/decade.</p> </div> <p>(1) <math>\frac{1}{(S+1)}</math> (2) <math>\frac{10}{(S+1)}</math> (3) <math>\frac{1}{S(S+1)}</math> (4) <math>\frac{.10}{s(s+1)}</math></p>








Question No.	Questions
21.	The octal equivalent of Hexadecimal number 2E.C1 would be (1) 212.602 (2) 56.602 (3) 56.623 (4) 65.302
22.	The complement of complement of $\bar{A}B + A\bar{B}$ will be (1) $AB + \bar{A}\bar{B}$ (2) $\bar{A}B$ (3) $\bar{A}B + A\bar{B}$ (4) $\bar{A}B \cdot (\bar{A} + B)$
23.	What is minimum number of 2-input NAND gates required to complement a 2-input OR gate (1) 2 (2) 4 (3) 3 (4) 5
24.	A basic CMOS two input NAND gate requires (1) Two N-channel MOSFETs (2) Two N-Channel & two P-channel MOSFETs (3) Two P-Channel MOSFETs (4) One N-Channel and one P-channel MOSFET
25.	IC 7402 is a – 2 input (1) NAND gate (2) EX-OR gate (3) NOR gate (4) OR Gate
26.	A decoder is nothing but a DEMUX without (1) control inputs (2) data input (3) enable input (4) clock
27.	The size of a PROM needed to implement a dual 8 to 1 MUX with common selection inputs would be (1) 256 K × 2 (2) 512 K × 2 (3) 1024 K × 2 (4) 128 K × 2

Question No.	Questions
28.	<p>Which one of following is not a synchronous input with reference to a flip flop</p> <p>(1) J input in JK flip flop                      (2) R input in RS flip flop  (3) Preset input in JK flip flop                (4) D-input in a D flip flop</p>
29.	<p>A counter having a modulus of 64 should have a minimum of</p> <p>(1) Six flip flops                                      (2) Seven flip flops  (3) 5 - D - flip flops                                (4) 64 flip flops</p>
30.	<p>A logic circuit that gives a pulsed waveform at the output for a sinusoidal input</p> <p>(1) Bi stable multivibrator                      (2) Monostable multivibrator  (3) Astable multivibrator                         (4) Schmitt trigger</p>
31.	<p>Current density in a semiconductor material is given by</p> <p>(1) <math>J = n \mu_n q/E</math>                                      (2) <math>J = p \mu_p q/E</math>  (3) <math>J = (n \mu_n + p \mu_p) \cdot E</math>                        (4) <math>J = (n \mu_n + p \mu_p) / E</math></p>
32.	<p>Fermi Level for a P-type semiconductor is given by</p> <p>(1) <math>E_F = E_V - KT \ln \frac{N_A}{N_V}</math>                      (2) <math>E_F = -E_V + KT \ln \frac{N_A}{N_V}</math>  (3) <math>E_F = E_V - K_T \ln \frac{N_A}{N_V}</math>                      (4) <math>E_F = E_C - K_T \ln \frac{N_C}{N_D}</math></p>
33.	<p>For conductors the value of Hall coefficient is given by</p> <p>(1) <math>R_H = \frac{1}{nq}</math>    (2) <math>R_H = \frac{nq}{\mu_n}</math>  (3) <math>R_H = \frac{\mu_p}{nq}</math>    (4) <math>R_H = \frac{n\mu_n + p\mu_p}{q}</math></p>

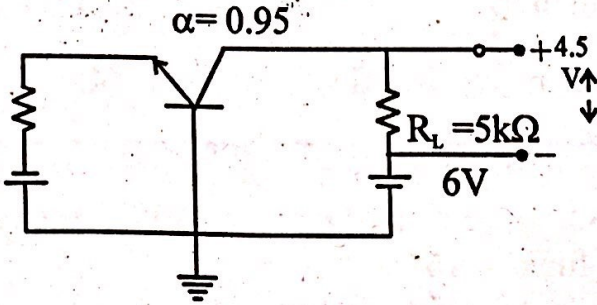

Question No.	Questions
34.	<p>The band gap energy of Ge at 300 K is given by</p> <p>(1) <math>E_g = 0.785 \text{ eV}</math>                      (2) <math>E_g = 1.121 \text{ eV}</math>  (3) <math>E_g = 0.7181 \text{ eV}</math>                      (4) <math>E_g = 1.212 \text{ eV}</math></p>
35.	<p>Under low level injection assumption, the injected minority current for an extrinsic semiconductor is essentially the</p> <p>(1) Diffusion current                      (2) Drift current  (3) Recombination current                      (4) Induction current</p>
36.	<p>Ga As has band gap energy of the order of</p> <p>(1) 1.43 eV                      (2) 0.7 eV  (3) 2.4 eV                      (4) 1.6 eV</p>
37.	<p>Typical value of impurity concentration in a tunnel diode is</p> <p>(1) 1 part in <math>10^8</math> parts                      (2) 1 part in <math>10^3</math> parts  (3) 1 PPM                      (4) 1 part in 10 parts</p>
38.	<p>In the given circuit, the value of collector current is :</p> <div style="text-align: center;">  </div> <p>(1) 0.8 mA                      (2) 0.9 mA  (3) 0.947 mA                      (4) 0.847 A</p>

Question No.	Questions
39.	MOSFET can be used as a (1) Current controlled capacitor      (2) Voltage controlled capacitor (3) Current controlled inductor      (4) Voltage controlled inductor
40.	The effective channel length of a MOSFET in saturation decreases with the increase in (1) Gate voltage      (2) Drain voltage (3) Source voltage      (4) Body voltage
41.	8086 has basic no. of instructions (1) 64      (2) 117 (3) 128      (4) 256
42.	The starting address of an interrupt is called (in 8086 Micro processor) (1) stack pointer      (2) program counter (3) interrupt output      (4) interrupt vector
43.	In 8086 type O interrupt is reserved for (1) single step      (2) NMI (3) Interrupt on overflow      (4) Divide Error
44.	For a fully controlled single phase converter supplies power to a resistive load of $10\Omega$ , the input voltage is 230 V, 50 Hz, the value of average output voltage is for $\alpha = 45^\circ$ (1) 276.74 V      (2) 376.74 V (3) 176.74 V      (4) 76.74 V













Question No.	Questions
63.	<p>Normal probability curve is denoted by</p> <p>(1) <math>\frac{1}{\sigma\sqrt{2\pi}} \exp(x^2 / 2\sigma^2)</math>                      (2) <math>\frac{1}{\sigma\sqrt{2\pi}} e^{x^2/2\sigma^2}</math></p> <p>(3) <math>\frac{1}{\sigma\sqrt{2\pi}} \exp(-x^2 / 2\sigma^2)</math>                      (4) <math>\frac{1}{\sigma\sqrt{2\pi}} \exp(x^3 / 2\sigma^3)</math></p>
64.	<p>Relative static error may be defined as</p> <p>(1) <math>\frac{\text{true value}}{\text{Absolute Error}}</math>                      (2) <math>\frac{\text{true value} - \text{Absolute Error}}{\text{true value}}</math></p> <p>(3) <math>\frac{\text{Absolute Error}}{\text{true value} + \text{Absolute Error}}</math>                      (4) <math>\frac{\text{Absolute Error}}{\text{true value}}</math></p>
65.	<p>Static sensitivity at an operating point is given by</p> <p>(1) <math>\frac{\text{infinitesimal change in the output}}{\text{infinitesimal change in the input}}</math></p> <p>(2) <math>\frac{\text{infinitesimal change in the input}}{\text{infinitesimal change in the output}}</math></p> <p>(3) <math>\frac{\text{true value}}{\text{Absolute value}}</math></p> <p>(4) <math>\frac{\text{Absolute value}}{\text{true value}}</math></p>
66.	<p>The input impedance of a cathode ray oscilloscope is of the order of</p> <p>(1) 10 <math>\Omega</math>                      (2) Mega ohms</p> <p>(3) Kilo ohms                      (4) fraction of 1 ohms</p>







Question No.	Questions
73.	<p>The divergence of a vector <math>\bar{A} = x \hat{a}_x + y \hat{a}_y + z \hat{a}_z</math> is</p> <p>(1) 0 (2) <math>\frac{1}{3}</math>  (3) 1 (4) 3</p>
74.	<p>Which of the following expression is true for a perfect dielectric</p> <p>(1) <math>\sigma \gg \omega \epsilon</math> (2) <math>\sigma = \omega \epsilon</math>  (3) <math>\sigma \ll \omega \epsilon</math> (4) <math>\sigma = \sqrt{\omega \epsilon}</math></p>
75.	<p>Given that <math>\sigma = 38 \text{ m S/m}</math> &amp; <math>\mu_r = 1</math> for aluminium, the skin depth at a frequency of 2 MHz would be equal to</p> <p>(1) 64.5 nm (2) 64.5 <math>\mu\text{m}</math>  (3) 57.7 nm (4) 57.77 <math>\mu\text{m}</math></p>
76.	<p>The power density of solar radiation at a place is <math>1.2 \text{ kW/m}^2</math>. The approximate value of electric field corresponding to the incident solar power is given by</p> <p>(1) 950 V/m (2) 750 V/m  (3) 450 V/m (4) 475 V/m</p>
77.	<p>A plane wave in air impinges at <math>45^\circ</math> on a loss less dielectric. The transmitted wave propagates at an angle <math>30^\circ</math> with respect to the normal. The value of dielectric constant of the dielectric is</p> <p>(1) 2.5 (2) 2.0  (3) 3.0 (4) 4.0</p>
78.	<p>A plane wave travelling in a free space is incident normally on a medium having <math>\epsilon_r = 4.0</math>. The fraction of power transmitted in to the medium is given by</p> <p>(1) <math>\frac{8}{9}</math> (2) <math>\frac{1}{2}</math>  (3) <math>\frac{1}{3}</math> (4) <math>\frac{5}{6}</math></p>














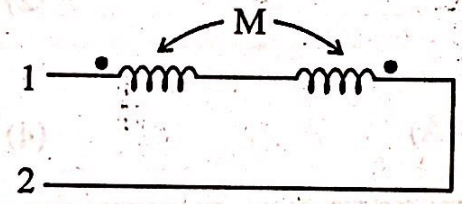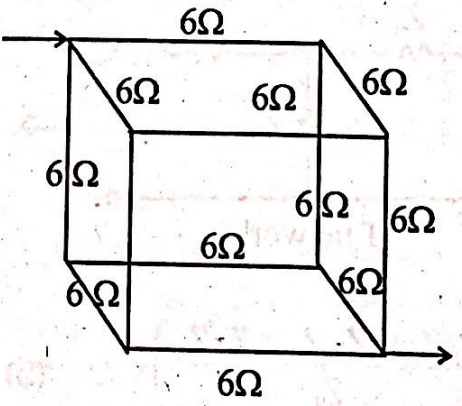

Question No.	Questions
92.	<p>In the above question <math>\pi</math> to T conversion gives the value of <math>Z_1</math></p> <p>(1) <math>\frac{Z_B Z_C}{Z_A + Z_B + Z_C}</math>                      (2) <math>\frac{Z_A + Z_B + Z_C}{Z_A Z_B + Z_B Z_C + Z_C Z_A}</math></p> <p>(3) <math>\frac{Z_1 + Z_2}{Z_1 + Z_2 + Z_3}</math>                      (4) <math>\frac{Z_A Z_B}{Z_A + Z_B + Z_C}</math></p>
93.	<p>The equivalent inductance of the following is given by</p> <div style="text-align: center;">  </div> <p>(1) <math>L_1 + L_2 + M</math>                      (2) <math>L_1 + L_2 - M</math></p> <p>(3) <math>L_1 + L_2 + 2M</math>                      (4) <math>L_1 + L_2 - 2M</math></p>
94.	<p>Every arm of the cube has a resistance of 6 ohms. The equivalent resistance of the cube is given by</p> <div style="text-align: center;">  </div> <p>(1) <math>36 \Omega</math>                      (2) <math>12 \Omega</math></p> <p>(3) <math>10 \Omega</math>                      (4) <math>5 \Omega</math></p>



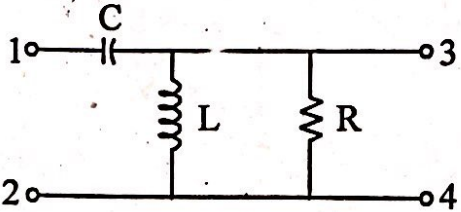

Question No.	Questions
99.	<p>The network shown behaves like a</p>  <p>(1) High pass filter                      (2) LPF (3) BPF                                      (4) Band stop filter</p>
100.	<p>If the scattering matrix <math>[S]</math> of a two port network is</p> $[S] = \begin{bmatrix} 0.2 \angle 0^\circ & 0.9 \angle 90^\circ \\ 0.9 \angle 90^\circ & 0.1 \angle 90^\circ \end{bmatrix}$ <p>then the network is</p> <p>(1) lossless and reciprocal              (2) lossless but non reciprocal (3) lossy but reciprocal                  (4) neither lossy nor reciprocal</p>



Maharshi Dayanand University Rohtak

Deptt. of ECE

M. Phil/ PhD/URS Entrance Examination Answer Key

Sr. No.	Set-A	Set-B	Set-C	Set-D
1	A	C	C	C
2	D	A	B	B
3	D	A	D	D
4	D	C	C	C
5	B	A	D	D
6	B	A	A	C
7	B	C	B	A
8	B	B	A	D
9	A	B	B	C
10	C	B	C	A
11	C	B	A	D
12	A	D	B	A
13	A	D	A	B
14	C	C	A	B
15	A	B	D	B
16	A	D	B	B
17	C	D	C	A
18	B	C	A	D
19	B	D	D	B
20	B	A	B	C
21	A	C	A	B
22	B	B	D	C
23	A	D	D	C
24	A	C	D	B
25	D	D	B	C
26	B	C	B	B
27	C	A	B	B
28	A	D	B	C
29	D	C	A	A
30	B	A	C	D
31	B	D	B	C
32	C	A	D	A
33	C	B	D	A
34	B	B	C	C
35	C	B	B	A
36	B	B	D	A
37	B	A	D	C
38	C	D	C	B
39	A	B	D	B
40	D	C	A	B
41	C	B	C	B
42	B	C	A	D
43	D	C	C	D
44	C	B	C	C
45	D	C	D	B
46	A	B	C	D
47	B	B	B	D
48	A	C	B	C
49	B	A	A	D
50	C	D	A	A

Maharshi Dayanand University Rohtak

Deptt. of ECE

M. Phil/ PhD/URS Entrance Examination Answer Key

Sr. No.	Set-A	Set-B	Set-C	Set-D
51	D	A	B	C
52	A	B	C	A
53	B	A	C	C
54	B	A	B	C
55	B	D	C	D
56	B	B	B	C
57	A	C	B	B
58	D	A	C	B
59	B	D	A	A
60	C	B	D	A
61	C	C	C	A
62	A	B	B	A
63	C	D	D	C
64	C	C	C	D
65	D	D	D	A
66	C	A	C	B
67	B	B	A	A
68	B	A	D	C
69	A	B	C	C
70	A	C	A	A
71	C	C	A	C
72	B	A	A	B
73	D	C	C	D
74	C	C	D	C
75	D	D	A	D
76	C	C	B	A
77	A	B	A	B
78	D	B	C	A
79	C	A	C	B
80	A	A	A	C
81	A	A	C	A
82	A	D	A	B
83	C	D	A	A
84	D	D	C	A
85	A	B	A	D
86	B	B	A	B
87	A	B	C	C
88	C	B	B	A
89	C	A	B	D
90	A	C	B	B
91	B	A	D	A
92	D	A	A	D
93	D	C	B	D
94	C	D	B	D
95	B	A	B	B
96	D	B	B	B
97	D	A	A	B
98	C	C	D	B
99	D	C	B	A
100	A	A	C	C

*[Signature]*  
20/11/18

*[Signature]*  
20-11-18

*[Signature]*  
20/11/18