

(Set-“X”)

(DO NOT OPEN THIS QUESTION BOOKLET BEFORE TIME OR UNTIL YOU ARE ASKED TO DO SO)

(M.Phil/Ph.D/URS-EE-2018)

Code **A**

Subject : ELECTRICAL ENGG.

Sr. No. 100021

Time : 1½ Hours

Max. Marks : 100

Total Questions : 100

Roll No. _____ (in figure) _____ (in words)

Name : _____ Father's Name : _____

Mother's Name : _____ Date of Examination : _____

(Signature of the candidate)

(Signature of the Invigilator)

CANDIDATES MUST READ THE FOLLOWING INFORMATION/ INSTRUCTIONS BEFORE STARTING THE QUESTION PAPER.





1. All questions are compulsory.
2. The candidates must return the Question book-let as well as OMR answer-sheet to the Invigilator concerned before leaving the Examination Hall, failing which a case of use of unfair-means / mis-behaviour will be registered against him / her, in addition to lodging of an FIR with the police. Further the answer-sheet of such a candidate will not be evaluated.
3. Keeping in view the transparency of the examination system, carbonless OMR Sheet is provided to the candidate so that a copy of OMR Sheet may be kept by the candidate.
4. Question Booklet along with answer key of all the A, B, C, D code will be got uploaded on the University website after the conduct of Entrance Examination. In case there is any discrepancy in the Question Booklet / Answer Key, the same may be brought to the notice of the Controller of Examination in writing / through E.Mail within 24 hours of uploading the same on the University Website. Thereafter, no complaint in any case, will be considered
5. The candidate **MUST NOT** do any rough work or writing in the OMR Answer-Sheet. Rough work, if any, may be done in the question book-let itself. Answers **MUST NOT** be ticked in the Question book-let.
6. There will be no Negative marking. Each correct answer will be awarded one full mark. Cutting, erasing, overwriting and more than one answer in OMR Answer-Sheet will be treated as incorrect answer.
7. Use only Black or Blue **BALL POINT PEN** of good quality in the OMR Answer-Sheet.
8. **BEFORE ANSWERING THE QUESTIONS, THE CANDIDATES SHOULD ENSURE THAT THEY HAVE BEEN SUPPLIED CORRECT AND COMPLETE BOOK-LET. COMPLAINTS, IF ANY, REGARDING MISPRINTING ETC. WILL NOT BE ENTERTAINED 30 MINUTES AFTER STARTING OF THE EXAMINATION.**



Question No.	Questions
4.	<p>If $\delta(t)$ denotes a unit impulse then Laplace Transform of $\frac{d^2 \delta(t)}{dt^2}$ will be</p> <p>(1) 1 (2) s^2 (3) s (4) s^{-2}</p>
5.	<p>The state equation of LTI system is represented by</p> $\dot{x} = \begin{bmatrix} 0 & 0 \\ -2 & -1 \end{bmatrix} x + \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} u$ <p>The Eigen values are</p> <p>(1) $-1, +1$ (2) $0.5 \pm j 1.323$ (3) $-1, -1$ (4) None</p>
6.	<p>Line integral can be transformed into a surface integral by using</p> <p>(1) Divergence theorem (2) Gauss theorem (3) Stokes theorem (4) None of these</p>
7.	<p>Four fundamental equations of electromagnetics are known as</p> <p>(1) Fleming's laws (2) Faraday's laws (3) Lorentz equations (4) Maxwell's equations</p>
8.	<p>For a linear electromagnetic circuit, which of the following statements is true ?</p> <p>(1) Field energy is equal to the co-energy (2) Field energy is greater than the co-energy (3) Field energy is lesser than the co-energy (4) Co-energy is zero</p>

Question No.	Questions
13.	<p>A conductor of length L has current I passing through it, when it is placed parallel to strong magnetic field. The force experienced by the conductor will be</p> <p>(1) BIL (2) BIL^2 (3) BI^2L (4) Zero</p>
14.	<p>Cork Screw rule is used to find</p> <p>(1) Direction of magnetic field (2) Direction of electric field (3) Direction of current (4) Direction of emf</p>
15.	<p>A point pole has a strength of $4\pi \times 10^{-4}$ weber. The force in Newtons on a point pole of $4\pi \times 1.5 \times 10^{-4}$ weber placed at a distance of 10 cm from it will be</p> <p>(1) 20N (2) 15N (3) 7.5N (4) 3.75N</p>
16.	<p>In a sample it is observed that a carrier takes $100\mu s$ to over a distance of 10 cm. If the applied external field is 10^4 V/cm; find the mobility</p> <p>(1) $10^7 \text{ cm}^2/\text{Vs}$ (2) $10^{-3} \text{ cm}^2/\text{Vs}$ (3) $10 \text{ cm}^2/\text{Vs}$ (4) $10^7 \text{ m}^2/\text{Vs}$</p>
17.	<p>The current gain of a bipolar transistor drops at high frequency because of</p> <p>(1) Transistor internal capacitances (2) High current effects in the base (3) Parasitic inductive elements (4) The Early effect</p>


Question No.	Questions
18.	<p>A transistor has $\alpha = 0.98$, then determine β.</p> <p>(1) 50 (2) 49 (3) 70 (4) None of the above</p>
19.	<p>The value of emitter capacitor CE in a multistage amplifier is about</p> <p>(1) $0.1\mu\text{F}$ (2) 100pF (3) $0.01\mu\text{F}$ (4) $50\mu\text{F}$</p>
20.	<p>The conduction loss versus device current characteristic of a power MOSFET is best</p> <p>(1) A parabola (2) A straight line (3) A rectangular hyperbola (4) An exponentially decaying function</p>
21.	<p>The hexadecimal equivalent of the octal number 171.62 is</p> <p>(1) 3C1.C0 (2) 79.C8 (3) 89.C7 (4) 97.8C</p>
22.	<p>Which of the following circuit can be used as parallel to series converter ?</p> <p>(1) Digital Counter (2) Decoder (3) De-multiplexer (4) Multiplexer</p>
23.	<p>How many flip-flops are required to construct a decade counter ?</p> <p>(1) 10 (2) 3 (3) 4 (4) 2</p>

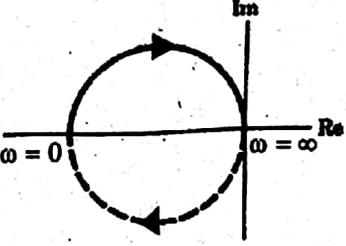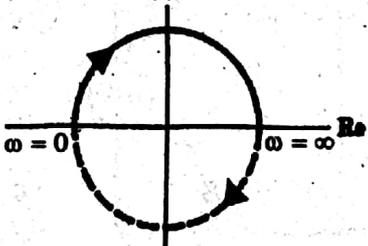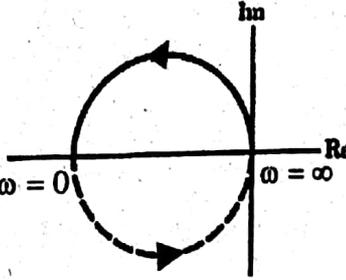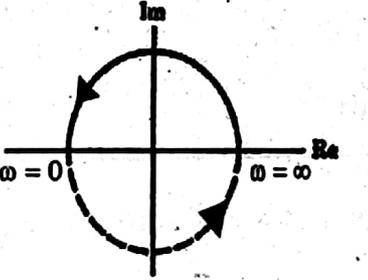Question No.	Questions
35.	<p>The open loop transfer function of a feedback system is</p> $G(s)H(s) = \frac{K(s+1)}{(1-s)}$ <p>The nyquist plot of this system is</p> <div style="display: flex; justify-content: space-around;"> <div style="text-align: center;"> <p>(1) </p> </div> <div style="text-align: center;"> <p>(2) </p> </div> </div> <div style="display: flex; justify-content: space-around; margin-top: 20px;"> <div style="text-align: center;"> <p>(3) </p> </div> <div style="text-align: center;"> <p>(4) </p> </div> </div>
36.	<p>The equation for 25 cycles electric current sine wave having rms value of 30 amps, will be</p> <div style="display: flex; justify-content: space-between;"> <div style="width: 45%;"> <p>(1) $42.4 \sin 50\pi t$</p> <p>(3) $30 \sin 25\pi t$</p> </div> <div style="width: 45%;"> <p>(2) $30 \sin 50\pi t$</p> <p>(4) $42.4 \sin 25\pi t$</p> </div> </div>
37.	<p>The equation of an emf is given by $e = I_m \left[\sqrt{(R^2 + 4\omega^2 L^2)} \right] \sin 2\omega t$. The amplitude of the wave will be</p> <div style="display: flex; justify-content: space-between;"> <div style="width: 45%;"> <p>(1) $I_m \left[(R^2 + 4\omega^2 L^2)^{1/2} \right]$</p> <p>(3) $\left[I_m (R^2 + 4\omega^2 L^2) \right]^{1/2}$</p> </div> <div style="width: 45%;"> <p>(2) $\sqrt{2} I_m \left[(R^2 + 4\omega^2 L^2)^{1/2} \right]$</p> <p>(4) $2 I_m \left[(R^2 + 4\omega^2 L^2)^{1/2} \right]$</p> </div> </div>

Question No.


Questions

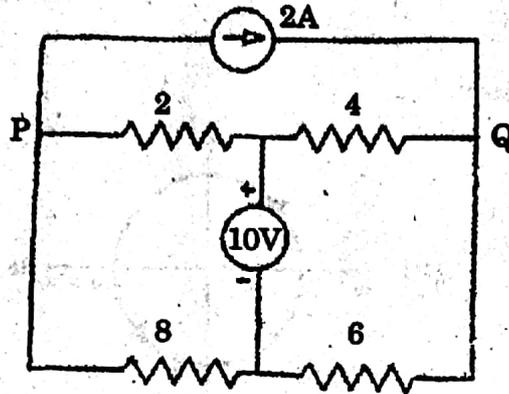38. In the figure, the potential difference between points P and Q is





- (1) 6
- (2) -6
- (3) 10
- (4) 12

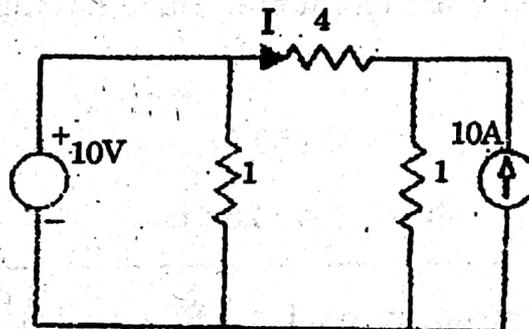39. In the network shown, what is the electric current I in the direction shown



- (1) 0 A.
- (2) 1/3 A.
- (3) 5/6 A.
- (4) 4 A.

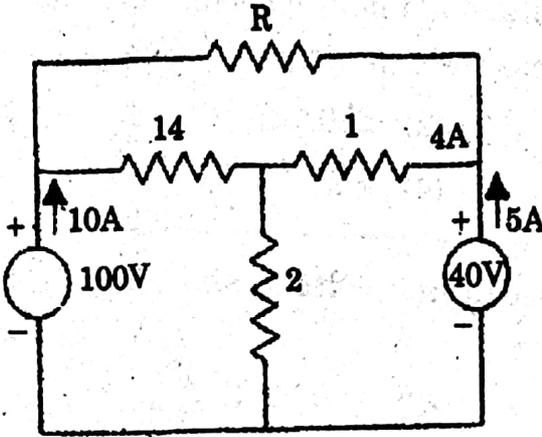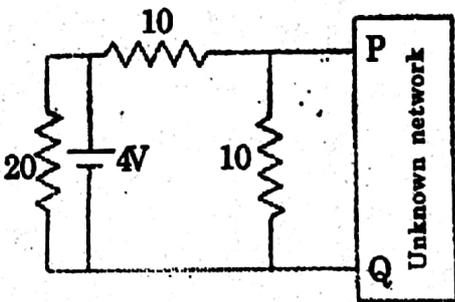Question No.	Questions
40.	<p>In the figure given, the value of R is</p>  <p>(1) $10\ \Omega$ (2) $12\ \Omega$ (3) $18\ \Omega$ (4) $24\ \Omega$</p>
41.	<p>In the given figure, the Thevenin equivalent voltage and impedance as seen from the terminals P-Q is given by</p>  <p>(1) 4 V and $7.5\ \Omega$ (2) 2 V and $7.5\ \Omega$ (3) 4 V and $5\ \Omega$ (4) 2 V and $5\ \Omega$</p>
42.	<p>A coil having a resistance of $5\ \Omega$ and inductance of $0.1\ \text{H}$ is connected in series with a condenser of capacitance $50\ \mu\text{F}$. A constant alternating voltage of $200\ \text{V}$ is applied to the circuit. The voltage across coil at resonance is</p> <p>(1) $200\ \text{V}$ (2) $1788\ \text{V}$ (3) $1800\ \text{V}$ (4) $2000\ \text{V}$</p>

Question No.

Questions

<p>52.</p>	<p>The dynamic characteristics of capacitive transducer are similar to those of.</p> <p>(1) low pass filter (2) high pass filter (3) notch filter (4) band stop filter</p>
<p>53.</p>	<p>The effect of error damping is to</p> <p>(1) provide larger settling time (2) delay the response (3) reduce steady state error (4) any of the above</p>
<p>54.</p>	<p>The bridge method commonly used for finding mutual inductance is</p> <p>(1) Heaviside Campbell bridge (2) Schering bridge (3) De Sauty's bridge (4) Wien bridge</p>
<p>55.</p>	<p>The bridge circuit shown in the figure below is used for the measurement of an unknown element Z_x. The bridge circuit is best suited when Z_x is a</p> <div data-bbox="383 1433 957 1780" data-label="Diagram"> </div> <p>(1) Lossy capacitor (2) Low Q inductor (3) High resistance (4) Low resistance</p>

Question No.	Questions
61.	<p>A rotating electrical machine having its self-inductance's of both the stator and the rotor windings independent of the rotor position will definitely not develop</p> <p>(1) Starting Torque (2) Synchronizing torque (3) Hysteresis Torque (4) Reluctance torque</p>
62.	<p>If peak value of phase mmf is F_{max}, then peak value of the rotating field caused by three phase is</p> <p>(1) $(3/2) F_{max}$ (2) F_{max} (3) $3 F_{max}$ (4) $(1/2) F_{max}$</p>
63.	<p>A 50 Hz, 4 pole turbo generator rated at 20 MVA, 13.2 KV has inertia constant $H = 3$ kW sec / KVA. The kinetic energy stored in the rotor is</p> <p>(1) 80 MJ (2) 60 MJ (3) 20 MJ (4) 10 MJ</p>
64.	<p>An alternator is supplying a load of 300 kW of a p.f. of 0.6 lagging. If the power factor is raised to unity. How many more kilowatts can alternator supply for the same KVA loading</p> <p>(1) 100 kW (2) 200 kW (3) 300 kW (4) 500 kW</p>
65.	<p>A 300 kVA, single phase transformer is designed to have resistance of 1.5 % and max. efficiency occurs at load of 173.2 kVA. When supplying the full load at 0.8 p.f. lagging at normal voltage, the efficiency will be</p> <p>(1) 12.6% (2) 97.6% (3) 35.5% (4) 29.6%</p>

Question No.	Questions
66.	<p>For constant load current at which power factor the efficiency of a transformer will be maximum ?</p> <ol style="list-style-type: none">(1) Zero power factor(2) Unity power factor(3) Leading power factor(4) Lagging power factor
67.	<p>The all-day efficiency is the term related to</p> <ol style="list-style-type: none">(1) Power transformer(2) Distribution transformer(3) Current transformer(4) Voltage transformer
68.	<p>Satisfactory commutation of DC machine requires</p> <ol style="list-style-type: none">(1) Smooth, concentric commutator properly undercut(2) Brushes should smoothly run in the holders(3) Brushes should be of proper grade and size(4) All of the above
69.	<p>In a 3 - Φ induction motor running at full load which of these parameters is stationary with respect to the stator mmf wave ?</p> <ol style="list-style-type: none">(1) Stator winding(2) Rotor winding(3) Both rotor and stator winding(4) Rotor mmf wave

Question No.	Questions
74.	<p>The area under load curve represents</p> <p>(1) System voltage (2) Current</p> <p>(3) Average demand (4) Maximum demand</p>
75.	<p>A power station supplies the peak load of 50 MW, 40 MW and 70 MW to three localities. The annual load factor is 0.50 p.u. and the diversity factor of the load at the station is 1.55 the maximum demand on the station and average load respectively will be</p> <p>(1) 51.61 MW (2) 57.5 MW</p> <p>(3) 53 MW (4) 52 MW</p>
76.	<p>Which of the following circuit breakers produce least arc energy ?</p> <p>(1) Air blast (2) Air break</p> <p>(3) Minimum oil (4) Plain oil</p>
77.	<p>A 100 Km long transmission line is loaded at 110 kV. If the loss of line is 5 MW and the load is 150 VA the resistance of the line is</p> <p>(1) 4.65 ohms / phase (2) 2.26 ohms / phase</p> <p>(3) 8.06 ohms / phase (4) 6.06 ohms / phase</p>
78.	<p>A three phase, 33 kV oil circuit breaker is rated 1200 A, 2000 MVA, 3 s. The symmetrical breaking current is</p> <p>(1) 1200 A (2) 3600 A</p> <p>(3) 35 kA (4) 104.8 kA</p>

Question No.	Questions
88.	Triacs cannot be used in AC voltage regulator for a (1) Resistive load (2) Inductive load (3) Back emf load (4) Resistive Inductive
89.	Latching current for an SCR inserted between a dc voltage source of 200 V and load is 100 mA. Compute the minimum rate of width pulse required to turn ON the SCR in case load consists of $R = 20 \Omega$ in series with $L = 0.2 \text{ H}$ (1) $200 \mu\text{s}$ (2) $300 \mu\text{s}$ (3) $150 \mu\text{s}$ (4) $100 \mu\text{s}$
90.	Delay time is defined by the interval when (1) gate current increases from 90% to 100% of its final value (2) anode current reaches 10% from forward leakage current (3) anode voltage drops from 100% to 90% of its actual value (4) all of these
91.	Typical range of thyristor turn OFF time is (1) $3 - 10 \mu\text{s}$ (2) $3 - 50 \mu\text{s}$ (3) $3 - 100 \mu\text{s}$ (4) $3 - 500 \mu\text{s}$

Question No.	Questions
92.	<p>String efficiency depends upon</p> <ol style="list-style-type: none">(1) voltage rating of whole string(2) no. of SCR in the string(3) voltage rating of one SCR(4) all of these
93.	<p>A thyristor string is made of a no. of SCR connected in series and parallel. The string have voltage and current of 11 KV and 4 KA. The voltage and current rating of available SCRs are 1800 V and 1000 A. For a string efficiency of 90% let the number of SCRs in series and parallel are a and b respectively. Then the value of a and b will be</p> <ol style="list-style-type: none">(1) 5, 7(2) 4, 6(3) 7, 5(4) 6, 4
94.	<p>A 200 A thyristor is to be operated in parallel with a 300 A thyristor. The ON state voltage drops are 1.5 V and 1.2 Volts. What is the value of resistance R to be connected in series with each thyristor, so that current through the combination is 500 A and each of them is fully loaded ?</p> <ol style="list-style-type: none">(1) $0.03 \times 10^{-2} \Omega$(2) $0.3 \times 10^{-3} \Omega$(3) $3.0 \times 10^{-3} \Omega$(4) $0.3 \times 10^{-2} \Omega$

(Set-“X”)

(DO NOT OPEN THIS QUESTION BOOKLET BEFORE TIME OR UNTIL YOU ARE ASKED TO DO SO)

(M.Phil/Ph.D/URS-EE-2018)

Code

B

Subject : ELECTRICAL ENGG.

Sr. No. ~~100018~~

Time : 1¼ Hours

Max. Marks : 100

Total Questions : 100

Roll No. _____ (in figure) _____ (in words)

Name : _____ Father's Name : _____

Mother's Name : _____ Date of Examination : _____


(Signature of the candidate)

(Signature of the Invigilator)


**CANDIDATES MUST READ THE FOLLOWING INFORMATION/
INSTRUCTIONS BEFORE STARTING THE QUESTION PAPER.**

1. All questions are compulsory.
2. The candidates must return the Question book-let as well as OMR answer-sheet to the Invigilator concerned before leaving the Examination Hall, failing which a case of use of unfair-means / mis-behaviour will be registered against him / her, in addition to lodging of an FIR with the police. Further the answer-sheet of such a candidate will not be evaluated.
3. Keeping in view the transparency of the examination system, carbonless OMR Sheet is provided to the candidate so that a copy of OMR Sheet may be kept by the candidate.
4. Question Booklet along with answer key of all the A, B, C, D code will be got uploaded on the University website after the conduct of Entrance Examination. In case there is any discrepancy in the Question Booklet / Answer Key, the same may be brought to the notice of the Controller of Examination in writing / through E.Mail within 24 hours of uploading the same on the University Website. Thereafter, no complaint in any case, will be considered
5. The candidate MUST NOT do any rough work or writing in the OMR Answer-Sheet. Rough work, if any, may be done in the question book-let itself. Answers MUST NOT be ticked in the Question book-let.
6. There will be no Negative marking. Each correct answer will be awarded one full mark. Cutting, erasing, overwriting and more than one answer in OMR Answer-Sheet will be treated as incorrect answer.
7. Use only Black or Blue **BALL POINT PEN** of good quality in the OMR Answer-Sheet.
8. BEFORE ANSWERING THE QUESTIONS, THE CANDIDATES SHOULD ENSURE THAT THEY HAVE BEEN SUPPLIED CORRECT AND COMPLETE BOOK-LET. COMPLAINTS, IF ANY, REGARDING MISPRINTING ETC. WILL NOT BE ENTERTAINED 30 MINUTES AFTER STARTING OF THE EXAMINATION.

Confidential

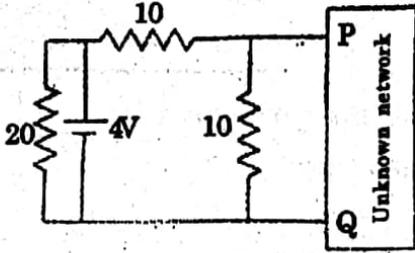Question No.	Questions
1.	<p>In the given figure, the Thevenin equivalent voltage and impedance as seen from the terminals P-Q is given by</p>  <p>(1) 4 V and 7.5 Ω (2) 2 V and 7.5 Ω (3) 4 V and 5 Ω (4) 2 V and 5 Ω</p>
2.	<p>A coil having a resistance of 5 Ω and inductance of 0.1 H is connected in series with a condenser of capacitance 50 μF. A constant alternating voltage of 200 V is applied to the circuit. The voltage across coil at resonance is</p> <p>(1) 200 V (2) 1788 V (3) 1800 V (4) 2000 V</p>
3.	<p>An RLC series circuit resonates at a frequency ω_r the ratio of $\omega_r L/R = 10$ the variable frequency voltage applied to the circuit is $20 \sin(\omega t + \pi/3)$ the voltage measured across the capacitance</p> <p>(1) $200/\sqrt{2}$ (2) $220/\sqrt{2}$ (3) $20/\sqrt{2}$ (4) $1/2$</p>
4.	<p>What is the relation between line voltage and phase voltage in case of delta connection ?</p> <p>(1) $V_L = V_p$ (2) $V_t = 1/\sqrt{3} V_p$ (3) $V_L = \sqrt{3} V_p$ (4) None of these</p>

Question No.	Questions
34.	If $\delta(t)$ denotes a unit impulse then Laplace Transform of $\frac{d^2 \delta(t)}{dt^2}$ will be (1) l (2) s^2 (3) s (4) s^{-2}
35.	The state equation of LTI system is represented by $\dot{x} = \begin{bmatrix} 0 & 0 \\ -2 & -1 \end{bmatrix} x + \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} u$ The Eigen values are (1) $-1, +1$ (2) $0.5 \pm j 1.323$ (3) $-1, -1$ (4) None
36.	Line integral can be transformed into a surface integral by using (1) Divergence theorem (2) Gauss theorem (3) Stokes theorem (4) None of these
37.	Four fundamental equations of electromagnetics are known as (1) Fleming's laws (2) Faraday's laws (3) Lorentz equations (4) Maxwell's equations
38.	For a linear electromagnetic circuit, which of the following statements is true ? (1) Field energy is equal to the co-energy (2) Field energy is greater than the co-energy (3) Field energy is lesser than the co-energy (4) Co-energy is zero

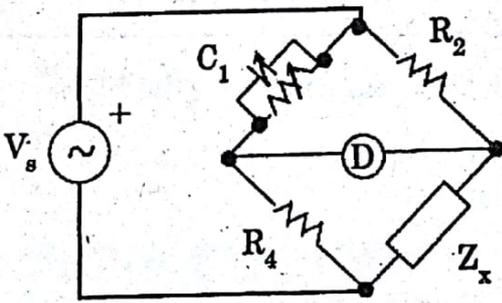Question No.	Questions
43.	<p>The effect of error damping is to</p> <ol style="list-style-type: none"> (1) provide larger settling time (2) delay the response (3) reduce steady state error (4) any of the above
44.	<p>The bridge method commonly used for finding mutual inductance is</p> <ol style="list-style-type: none"> (1) Heaviside Campbell bridge (2) Schering bridge (3) De Sauty's bridge (4) Wien bridge
45.	<p>The bridge circuit shown in the figure below is used for the measurement of an unknown element Z_x. The bridge circuit is best suited when Z_x is a</p> <div style="text-align: center;">  </div> <ol style="list-style-type: none"> (1) Lossy capacitor (2) Low Q inductor (3) High resistance (4) Low resistance

Code-B

Question No.	Questions
59.	<p>In a 3-Φ induction motor running at full load which of these parameters is stationary with respect to the stator mmf wave ?</p> <p>(1) Stator winding (2) Rotor winding (3) Both rotor and stator winding (4) Rotor mmf wave</p>
60.	<p>The damper windings also called the squirrel cage winging's damper grids</p> <p>(1) consists of short-circuited copper bars embedded in the field pole faces (2) are provided in a synchronous motor to make itself starting (3) are provided on the stator for improving power factor (4) both (1) and (2)</p>
61.	<p>The hexadecimal equivalent of the octal number 171.62 is</p> <p>(1) 3C1.C0 (2) 79.C8 (3) 89.C7 (4) 97.8C</p>
62.	<p>Which of the following circuit can be used as parallel to series converter ?</p> <p>(1) Digital Counter (2) Decoder (3) De-multiplexer (4) Multiplexer</p>
63.	<p>How many fillip-flops are required to construct a decade counter ?</p> <p>(1) 10 (2) 3 (3) 4 (4) 2</p>

Question No.	Questions
76.	<p>In a sample it is observed that a carrier takes $100\mu\text{s}$ to over a distance of 10 cm. If the applied external field is 10^4 V/cm; find the mobility</p> <p>(1) $10^7\text{ cm}^2/\text{Vs}$ (2) $10^{-3}\text{ cm}^2/\text{Vs}$ (3) $10\text{ cm}^2/\text{Vs}$ (4) $10^7\text{ m}^2/\text{Vs}$</p>
77.	<p>The current gain of a bipolar transistor drops at high frequency because of</p> <p>(1) Transistor internal capacitances (2) High current effects in the base (3) Parasitic inductive elements (4) The Early effect</p>
78.	<p>A transistor has $\alpha = 0.98$, then determine β.</p> <p>(1) 50 (2) 49 (3) 70 (4) None of the above</p>
79.	<p>The value of emitter capacitor CE in a multistage amplifier is about</p> <p>(1) $0.1\mu\text{F}$ (2) 100pF (3) $0.01\mu\text{F}$ (4) $50\mu\text{F}$</p>
80.	<p>The conduction loss versus device current characteristic of a power MOSFET is best</p> <p>(1) A parabola (2) A straight line (3) A rectangular hyperbola (4) An exponentially decaying function</p>

Question No.	Questions
81.	Mho relay is used for the protection of (1) medium length lines (2) long transmission lines (3) short length lines (4) no length criterion
82.	An overhead line conductor has an inductance per unit length of L henry. If the entire medium around the conductor is filled with a dielectric material of permittivity ϵ , then the inductance will (1) L/ϵ (2) $L/0.5\epsilon$ (3) L (4) unchanged
83.	When a line-to-ground fault occurs, the current in the phase is 100 A. The zero sequence current in the case will be (1) 33.3 A (2) 0 A (3) 66.6 A (4) 99.9 A
84.	Air blast circuit breaker is most suitably used in (1) Up to 132 KV line (2) Up to 260 KV line (3) Up to 400 KV line (4) any voltage
85.	To reduce the adverse effect of corona discharge which conductor is specially used ? (1) ACSR (2) Bundle conductor (3) Aluminium conductor (4) Copper conductor


Question No.	Questions
86.	<p>A single phase one pulse controlled circuit has a resistance R and counter emf E load $400 \sin(314t)$ as the source voltage. For a load counter emf of 200 V, the range of firing angle control is</p> <p>(1) 30° to 150° (2) 30° to 180° (3) 60° to 120° (4) 60° to 180°</p>
87.	<p>Let of a thyristor V_{c1}, V_{c2}, V_{c3} are forward break over voltage for gate current I_{g1}, I_{g2}, I_{g3} respectively. Then</p> <p>(1) $V_{c1} > V_{c2} > V_{c3}$ when $I_{g1} > I_{g2} > I_{g3}$ (2) $V_{c1} > V_{c2} > V_{c3}$ when $I_{g1} < I_{g2} < I_{g3}$ (3) $V_{c1} = V_{c2} = V_{c3}$ any value of I_g (4) $V_{c1} > V_{c2} > V_{c3}$ when $I_{g1} \geq I_{g2} \geq I_{g3}$</p>
88.	<p>Triacs cannot be used in AC voltage regulator for a</p> <p>(1) Resistive load (2) Inductive load (3) Back emf load (4) Resistive Inductive</p>
89.	<p>Latching current for an SCR inserted between a dc voltage source of 200 V and load is 100 mA. Compute the minimum rate of width pulse required to turn ON the SCR in case load consists of $R = 20 \Omega$ in series with $L = 0.2$ H</p> <p>(1) $200 \mu s$ (2) $300 \mu s$ (3) $150 \mu s$ (4) $100 \mu s$</p>

Question No.

Questions

90. Delay time is defined by the interval when
- (1) gate current increases from 90% to 100% of its final value
 - (2) anode current reaches 10% from forward leakage current
 - (3) anode voltage drops from 100% to 90% of its actual value
 - (4) all of these

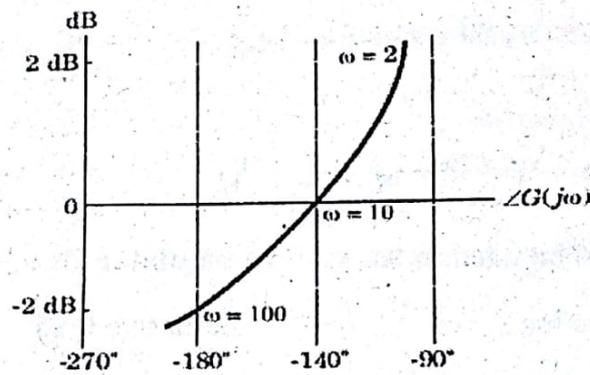91. Consider the gain-phase plot shown in fig. The gain margin and phase margin are






Fig

- (1) -2 dB, 40°
- (2) 2 dB, 40°
- (3) 2 dB, 140°
- (4) -2 dB, 140°

92. The root locus of a unity feed function is given by

- (1) $k/s(s+1)(s+2)$
- (2) $k(s+1)/s(s+2)$
- (3) $k(s+2)/s(s+1)$
- (4) $ks/(s+1)(s+2)$

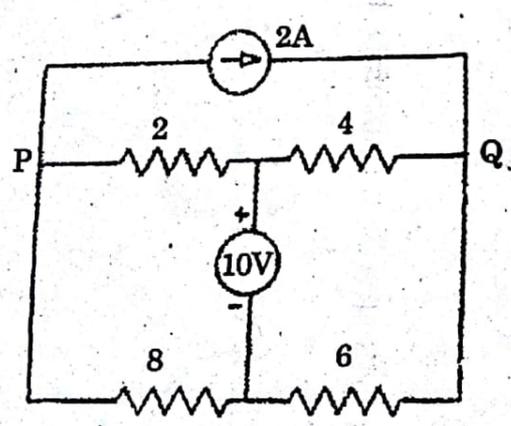Question No.	Questions
96.	<p>The equation for 25 cycles electric current sine wave having rms value of 30 amps, will be</p> <p>(1) $42.4 \sin 50 \pi t$ (2) $30 \sin 50 \pi t$ (3) $30 \sin 25 \pi t$ (4) $42.4 \sin 25 \pi t$</p>
97.	<p>The equation of an emf is given by $e = I_m [\sqrt{(R^2 + 4\omega^2 L^2)}] \sin 2\omega t$. The amplitude of the wave will be</p> <p>(1) $I_m [(R^2 + 4\omega^2 L^2)^{1/2}]$ (2) $\sqrt{2} I_m [(R^2 + 4\omega^2 L^2)^{1/2}]$ (3) $[I_m (R^2 + 4\omega^2 L^2)]^{1/2}$ (4) $2 I_m [(R^2 + 4\omega^2 L^2)^{1/2}]$</p>
98.	<p>In the figure, the potential difference between points P and Q is</p>  <p>(1) 6 (2) -6 (3) 10 (4) 12</p>

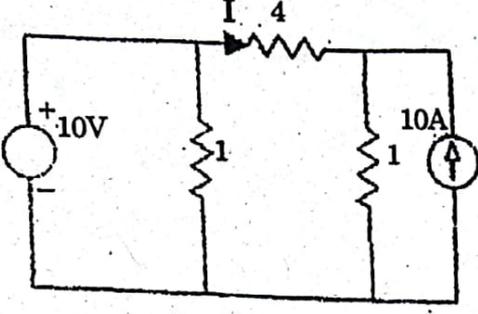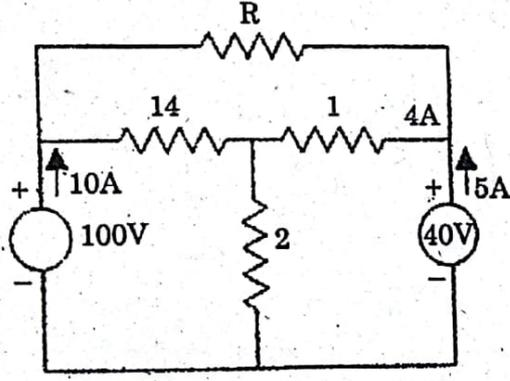Question No.	Questions
99.	<p>In the network shown, what is the electric current I in the direction shown</p>  <p>(1) 0 A. (2) $1/3$ A. (3) $5/6$ A. (4) 4 A.</p>
100.	<p>In the figure given, the value of R is</p>  <p>(1) 10Ω (2) 12Ω (3) 18Ω (4) 24Ω</p>

(Set-“X”)

(DO NOT OPEN THIS QUESTION BOOKLET BEFORE TIME OR UNTIL YOU ARE ASKED TO DO SO)

(M.Phil/Ph.D/URS-EE-2018)

Code

C

Subject : ELECTRICAL ENGG.

Sr. No. **100023**

Time : 1¼ Hours

Max. Marks : 100

Total Questions : 100

Roll No. _____ (in figure) _____ (in words)

Name : _____ Father's Name : _____

Mother's Name : _____ Date of Examination : _____

(Signature of the candidate)


(Signature of the Invigilator)


**CANDIDATES MUST READ THE FOLLOWING INFORMATION/
INSTRUCTIONS BEFORE STARTING THE QUESTION PAPER.**

1. All questions are compulsory.
2. The candidates must return the Question book-let as well as OMR answer-sheet to the Invigilator concerned before leaving the Examination Hall, failing which a case of use of unfair-means / mis-behaviour will be registered against him / her, in addition to lodging of an FIR with the police. Further the answer-sheet of such a candidate will not be evaluated.
3. Keeping in view the transparency of the examination system, carbonless OMR Sheet is provided to the candidate so that a copy of OMR Sheet may be kept by the candidate.
4. Question Booklet along with answer key of all the A, B, C, D code will be got uploaded on the University website after the conduct of Entrance Examination. In case there is any discrepancy in the Question Booklet / Answer Key, the same may be brought to the notice of the Controller of Examination in writing / through E.Mail within 24 hours of uploading the same on the University Website. Thereafter, no complaint in any case, will be considered
5. The candidate **MUST NOT** do any rough work or writing in the OMR Answer-Sheet. Rough work, if any, may be done in the question book-let itself. Answers **MUST NOT** be ticked in the Question book-let.
6. There will be no Negative marking. Each correct answer will be awarded one full mark. Cutting, erasing, overwriting and more than one answer in OMR Answer-Sheet will be treated as incorrect answer.
7. Use only Black or Blue **BALL POINT PEN** of good quality in the OMR Answer-Sheet.
8. **BEFORE ANSWERING THE QUESTIONS, THE CANDIDATES SHOULD ENSURE THAT THEY HAVE BEEN SUPPLIED CORRECT AND COMPLETE BOOK-LET. COMPLAINTS, IF ANY, REGARDING MISPRINTING ETC. WILL NOT BE ENTERTAINED 30 MINUTES AFTER STARTING OF THE EXAMINATION.**



Question No.	Questions
1.	The hexadecimal equivalent of the octal number 171.62 is (1) 3C1.C0 (2) 79.C8 (3) 89.C7 (4) 97.8C
2.	Which of the following circuit can be used as parallel to series converter ? (1) Digital Counter (2) Decoder (3) De-multiplexer (4) Multiplexer
3.	How many flip-flops are required to construct a decade counter ? (1) 10 (2) 3 (3) 4 (4) 2
4.	Which is not a type of ROM ? (1) Mask ROM (2) PROM (3) EEPROM (4) XROM
5.	A stage in shift register consist of (1) Latch (2) Flip flop (3) Byte of storage (4) four bits of storage
6.	The closed loop transfer function of a system is $T(s) = \frac{(s+8)(s+6)}{s^5 + s^4 + 4s^3 - 4s^2 + 3s - 2}$ The number of poles in RHP and LHP are (1) 4,1 (2) 1,4 (3) 3,2 (4) 2,3

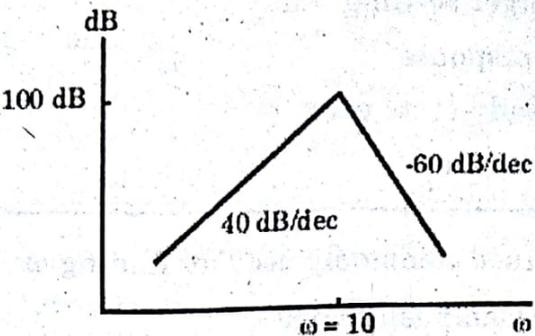Question No.	Questions
10.	<p>For the Bode plot shown in figure, the transfer function is</p>  <p>(1) $\frac{100 s^2}{(1+0.1s)^3}$</p> <p>(2) $\frac{1000 s^2}{(1+0.1s)^6}$</p> <p>(3) $\frac{15.6 s^2}{(1+0.1s)^6}$</p> <p>(4) None</p>
11.	<p>A psychrometric chart is used to determine</p> <p>(1) pH (2) Sound velocity in glasses</p> <p>(3) CO₂ concentration (4) Relative humidity</p>
12.	<p>The dynamic characteristics of capacitive transducer are similar to those of</p> <p>(1) low pass filter (2) high pass filter</p> <p>(3) notch filter (4) band stop filter</p>

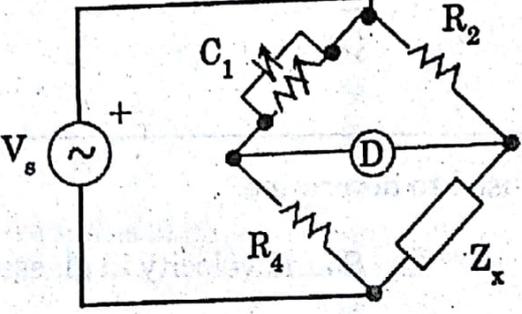Question No.	Questions
13.	<p>The effect of error damping is to</p> <ol style="list-style-type: none"> (1) provide larger settling time (2) delay the response (3) reduce steady state error (4) any of the above
14.	<p>The bridge method commonly used for finding mutual inductance is</p> <ol style="list-style-type: none"> (1) Heaviside Campbell bridge (2) Schering bridge (3) De Sauty's bridge (4) Wien bridge
15.	<p>The bridge circuit shown in the figure below is used for the measurement of an unknown element Z_x. The bridge circuit is best suited when Z_x is a</p>  <ol style="list-style-type: none"> (1) Lossy capacitor (2) Low Q inductor (3) High resistance (4) Low resistance

Question No.	Questions
21.	<p>Mho relay is used for the protection of</p> <p>(1) medium length lines (2) long transmission lines</p> <p>(3) short length lines (4) no length criterion</p>
22.	<p>An overhead line conductor has an inductance per unit length of L henry. If the entire medium around the conductor is filled with a dielectric material of permittivity ϵ, then the inductance will</p> <p>(1) L/ϵ (2) $L/0.5\epsilon$</p> <p>(3) L (4) unchanged</p>
23.	<p>When a line-to-ground fault occurs, the current in the phase is 100 A. The zero sequence current in the case will be</p> <p>(1) 33.3 A (2) 0 A</p> <p>(3) 66.6 A (4) 99.9 A</p>
24.	<p>Air blast circuit breaker is most suitably used in</p> <p>(1) Up to 132 KV line</p> <p>(2) Up to 260 KV line</p> <p>(3) Up to 400 KV line</p> <p>(4) any voltage</p>
25.	<p>To reduce the adverse effect of corona discharge which conductor is specially used ?</p> <p>(1) ACSR (2) Bundle conductor</p> <p>(3) Aluminium conductor (4) Copper conductor</p>

Question No.	Questions
26.	<p>A single phase one pulse controlled circuit has a resistance R and counter emf E load $400 \sin(314t)$ as the source voltage. For a load counter emf of 200 V, the range of firing angle control is</p> <p>(1) 30° to 150° (2) 30° to 180° (3) 60° to 120° (4) 60° to 180°</p>
27.	<p>Let of a thyristor V_{c1}, V_{c2}, V_{c3} are forward break over voltage for gate current I_{g1}, I_{g2}, I_{g3} respectively. Then</p> <p>(1) $V_{c1} > V_{c2} > V_{c3}$ when $I_{g1} > I_{g2} > I_{g3}$ (2) $V_{c1} > V_{c2} > V_{c3}$ when $I_{g1} < I_{g2} < I_{g3}$ (3) $V_{c1} = V_{c2} = V_{c3}$ any value of I_g (4) $V_{c1} > V_{c2} > V_{c3}$ when $I_{g1} \geq I_{g2} \geq I_{g3}$</p>
28.	<p>Triacs cannot be used in AC voltage regulator for a</p> <p>(1) Resistive load (2) Inductive load (3) Back emf load (4) Resistive Inductive</p>
29.	<p>Latching current for an SCR inserted between a dc voltage source of 200 V and load is 100 mA. Compute the minimum rate of width pulse required to turn ON the SCR in case load consists of $R = 20 \Omega$ in series with $L = 0.2 \text{ H}$</p> <p>(1) $200 \mu\text{s}$ (2) $300 \mu\text{s}$ (3) $150 \mu\text{s}$ (4) $100 \mu\text{s}$</p>



Question No.	Questions				
30.	<p>Delay time is defined by the interval when</p> <ol style="list-style-type: none"> (1) gate current increases from 90% to 100% of its final value (2) anode current reaches 10% from forward leakage current (3) anode voltage drops from 100% to 90% of its actual value (4) all of these 				
31.	<p>EHV transmission has which of the following advantages ?</p> <ol style="list-style-type: none"> (1) Reduction in noise (2) Increase in transmission efficiency (3) Improves voltage regulation (4) All of these 				
32.	<p>Absence of skin effect lower line cost, less corona effect are the features of which of the transmission system ?</p> <ol style="list-style-type: none"> (1) EHV – AC system (2) HVDC system (3) Both (1) and (2) (4) UHV – AC system 				
33.	<p>Inside the station of the broad gauge line what is the clearance between track and lowest conductor for operating voltages from 650 V– 3 kV ?</p> <table style="width: 100%; border: none;"> <tr> <td style="width: 50%;">(1) 10 m</td> <td style="width: 50%;">(2) 7.2 m</td> </tr> <tr> <td>(3) 8.6 m</td> <td>(4) 7.6 m</td> </tr> </table>	(1) 10 m	(2) 7.2 m	(3) 8.6 m	(4) 7.6 m
(1) 10 m	(2) 7.2 m				
(3) 8.6 m	(4) 7.6 m				


Question No.	Questions
34.	<p>The area under load curve represents</p> <p>(1) System voltage (2) Current</p> <p>(3) Average demand (4) Maximum demand</p>
35.	<p>A power station supplies the peak load of 50 MW, 40 MW and 70 MW to three localities. The annual load factor is 0.50 p.u. and the diversity factor of the load at the station is 1.55 the maximum demand on the station and average load respectively will be</p> <p>(1) 51.61 MW (2) 57.5 MW</p> <p>(3) 53 MW (4) 52 MW</p>
36.	<p>Which of the following circuit breakers produce least arc energy ?</p> <p>(1) Air blast (2) Air break</p> <p>(3) Minimum oil (4) Plain oil</p>
37.	<p>A 100 Km long transmission line is loaded at 110 kV. If the loss of line is 5 MW and the load is 150 VA the resistance of the line is</p> <p>(1) 4.65 ohms / phase (2) 2.26 ohms / phase</p> <p>(3) 8.06 ohms / phase (4) 6.06 ohms / phase</p>
38.	<p>A three phase, 33 kV oil circuit breaker is rated 1200 A, 2000 MVA, 3 s. The symmetrical breaking current is</p> <p>(1) 1200 A (2) 3600 A</p> <p>(3) 35 kA (4) 104.8 kA</p>

Question No.	Questions
42.	Eigen vector(s) of the matrix $\begin{bmatrix} 0 & 0 & \alpha \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$ is (are) (1) $(0, 0, \alpha)$ (2) $(\alpha, 0, 0)$ (3) $(0, 0, 1)$ (4) $(0, \alpha, 0)$
43.	Consider the z-transform $X(z) = 5z^2 + 4z^{-1} + 3$; $0 < z < \infty$. The inverse z-transform $x[n]$ is (1) $5\delta[n+2] + 3\delta[n] + 4\delta[n-1]$ (2) $5\delta[n-2] + 3\delta[n] + 4\delta[n+1]$ (3) $5u[n+2] + 3u[n] + 4u[n-1]$ (4) $5u[n-2] + 3u[n] + 4u[n+1]$
44.	If $\delta(t)$ denotes a unit impulse then Laplace Transform of $\frac{d^2 \delta(t)}{dt^2}$ will be (1) l (2) s^2 (3) s (4) s^{-2}
45.	The state equation of LTI system is represented by $\dot{\mathbf{x}} = \begin{bmatrix} 0 & 0 \\ -2 & -1 \end{bmatrix} \mathbf{x} + \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \mathbf{u}$ The Eigen values are (1) $-1, +1$ (2) $0.5 \pm j 1.323$ (3) $-1, -1$ (4) None

Question No.	Questions
46.	<p>Line integral can be transformed into a surface integral by using</p> <p>(1) Divergence theorem (2) Gauss theorem (3) Stokes theorem (4) None of these</p>
47.	<p>Four fundamental equations of electromagnetics are known as</p> <p>(1) Fleming's laws (2) Faraday's laws (3) Lorentz equations (4) Maxwell's equations</p>
48.	<p>For a linear electromagnetic circuit, which of the following statements is true ?</p> <p>(1) Field energy is equal to the co-energy (2) Field energy is greater than the co-energy (3) Field energy is lesser than the co-energy (4) Co-energy is zero</p>
49.	<p>Which of the following statements holds for the divergence of electric and magnetic flux</p> <p>(1) Both are zero (2) These are zero for static densities but non-zero for time varying densities. (3) It is zero for the electric flux density (4) It is zero for the magnetic flux density</p>

Question No.	Questions
53.	The transfer function $\frac{1+0.5s}{1+s}$ represents (1) Lag network (2) Lead network (3) Lag-lead Network (4) Proportional controller
54.	If the stability error for a step input and speed of the response be the criteria for design, the suitable controller will be (1) P Controller (2) PI Controller (3) PD Controller (4) PID Controller
55.	The open loop transfer function of a feedback system is $G(s)H(s) = \frac{K(s+1)}{(1-s)}$ The nyquist plot of this system is
(1)	
(2)	
(3)	
(4)	
56.	The equation for 25 cycles electric current sine wave having rms value of 30 amps, will be (1) $42.4 \sin 50\pi t$ (2) $30 \sin 50\pi t$ (3) $30 \sin 25\pi t$ (4) $42.4 \sin 25\pi t$

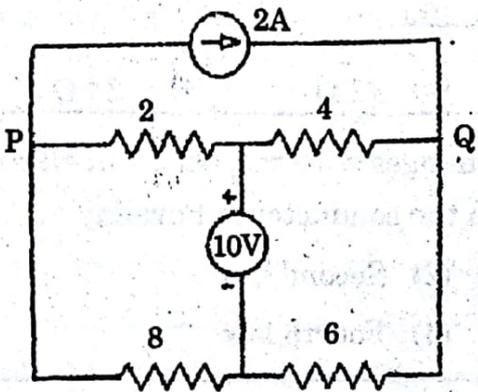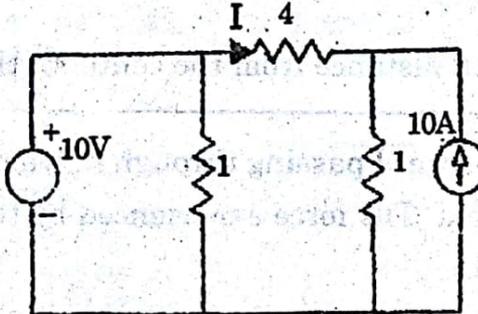
Question No.	Questions
57.	<p>The equation of an emf is given by $e = I_m \left[\sqrt{(R^2 + 4\omega^2 L^2)} \right] \sin 2\omega t$. The amplitude of the wave will be</p> <p>(1) $I_m \left[(R^2 + 4\omega^2 L^2)^{1/2} \right]$ (2) $\sqrt{2} I_m \left[(R^2 + 4\omega^2 L^2)^{1/2} \right]$</p> <p>(3) $\left[I_m (R^2 + 4\omega^2 L^2) \right]^{1/2}$ (4) $2 I_m \left[(R^2 + 4\omega^2 L^2)^{1/2} \right]$</p>
58.	<p>In the figure, the potential difference between points P and Q is</p>  <p>(1) 6 (2) -6 (3) 10 (4) 12</p>
59.	<p>In the network shown, what is the electric current I in the direction shown</p>  <p>(1) 0 A. (2) 1/3 A. (3) 5/6 A. (4) 4 A.</p>

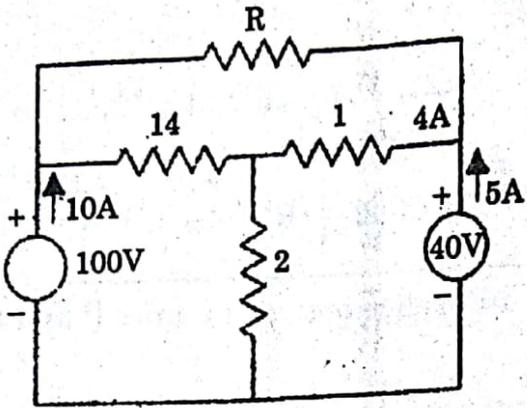Question No.	Questions
60.	<p>In the figure given, the value of R is</p>  <p>(1) $10\ \Omega$ (2) $12\ \Omega$ (3) $18\ \Omega$ (4) $24\ \Omega$</p>
61.	<p>Whenever the magnetic flux changes with respect to an electric conductor or a coil, an EMF is induced in the conductor is Faraday's</p> <p>(1) First law (2) Second law (3) Third law (4) Fourth law</p>
62.	<p>Inside a hollow conducting sphere</p> <p>(1) Electric field is zero. (2) Electric field is a non-zero constant. (3) Electric field changes with magnitude of the charge given to the conductor. (4) Electric field changes with distance from the center of the sphere.</p>
63.	<p>A conductor of length L has current I passing through it, when it is placed parallel to strong magnetic field. The force experienced by the conductor will be</p> <p>(1) BIL (2) BIL^2 (3) BI^2L (4) Zero</p>

Question No.	Questions
64.	Cork Screw rule is used to find (1) Direction of magnetic field (2) Direction of electric field (3) Direction of current (4) Direction of emf
65.	A point pole has a strength of $4\pi \times 10^{-4}$ weber. The force in Newtons on a point pole of $4\pi \times 1.5 \times 10^{-4}$ weber placed at a distance of 10 cm from it will be (1) 20N (2) 15N (3) 7.5N (4) 3.75N
66.	In a sample it is observed that a carrier takes $100\mu\text{s}$ to over a distance of 10 cm. If the applied external field is 10^4 V/cm; find the mobility (1) $10^7 \text{ cm}^2/\text{Vs}$ (2) $10^{-3} \text{ cm}^2/\text{Vs}$ (3) $10 \text{ cm}^2/\text{Vs}$ (4) $10^7 \text{ m}^2/\text{Vs}$
67.	The current gain of a bipolar transistor drops at high frequency because of (1) Transistor internal capacitances (2) High current effects in the base (3) Parasitic inductive elements (4) The Early effect
68.	A transistor has $\alpha = 0.98$, then determine β . (1) 50 (2) 49 (3) 70 (4) None of the above

Question No.	Questions
69.	<p>The value of emitter capacitor CE in a multistage amplifier is about</p> <p>(1) $0.1\mu\text{F}$ (2) 100pF (3) $0.01\mu\text{F}$ (4) $50\mu\text{F}$</p>
70.	<p>The conduction loss versus device current characteristic of a power MOSFET is best</p> <p>(1) A parabola (2) A straight line (3) A rectangular hyperbola (4) An exponentially decaying function</p>
71.	<p>In the given figure, the Thevenin equivalent voltage and impedance as seen from the terminals P-Q is given by</p>
(1)	4 V and $7.5\ \Omega$
(3)	4 V and $5\ \Omega$
(2)	2 V and $7.5\ \Omega$
(4)	2 V and $5\ \Omega$
72.	<p>A coil having a resistance of $5\ \Omega$ and inductance of $0.1\ \text{H}$ is connected in series with a condenser of capacitance $50\mu\text{F}$. A constant alternating voltage of $200\ \text{V}$ is applied to the circuit. The voltage across coil at resonance is</p> <p>(1) $200\ \text{V}$ (2) $1788\ \text{V}$ (3) $1800\ \text{V}$ (4) $2000\ \text{V}$</p>

Question No.	Questions
73.	<p>An RLC series circuit resonates at a frequency ω_r, the ratio of $\omega_r L/R = 10$ the variable frequency voltage applied to the circuit is $20 \sin(\omega t + \pi/3)$ the voltage measured across the capacitance</p> <p>(1) $200/\sqrt{2}$ (2) $220/\sqrt{2}$ (3) $20/\sqrt{2}$ (4) $1/2$</p>
74.	<p>What is the relation between line voltage and phase voltage in case of delta connection ?</p> <p>(1) $V_L = V_p$. (2) $V_t = 1/\sqrt{3} V_p$. (3) $V_L = \sqrt{3} V_p$. (4) None of these</p>
75.	<p>The rms value of the current in a wire which carries a dc current of 10 A and a sinusoidal alternating current of peak value 20 A is</p> <p>(1) 10 A (2) 14.14 A (3) 15 A (4) 17.32 A</p>
76.	<p>The purpose of compensation for a thermocouple is</p> <p>(1) To decrease temperature sensitivity (2) To increase voltage output (3) To cancel unwanted voltage output of a thermocouple (4) Used for high-temperature circuits</p>
77.	<p>Semiconductor strain gages typical have much higher gage factors than those of metallic strain gages primarily due to</p> <p>(1) Higher temperature sensitivity (2) Higher Poisson's ratio (3) Higher piezoresistive coefficient (4) Higher magnetostrictive coefficient</p>

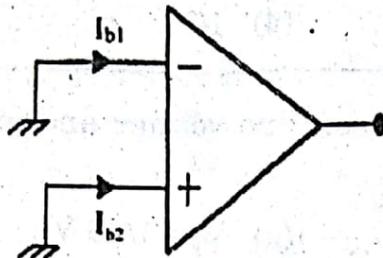Question No.	Questions
78.	<p>For the op-amp shown in the figure, the bias currents are $I_{b1} = 450 \text{ nA}$ and $I_{b2} = 350 \text{ nA}$. The values of the input bias current (I_b) and the input offset current (I_f) are</p>  <p>(1) $I_b = 800 \text{ nA}$, $I_f = 50 \text{ nA}$ (2) $I_b = 800 \text{ nA}$, $I_f = 100 \text{ nA}$ (3) $I_b = 400 \text{ nA}$, $I_f = 50 \text{ nA}$ (4) $I_b = 400 \text{ nA}$, $I_f = 100 \text{ nA}$</p>
79.	<p>A Hall Effect sensor</p> <p>(1) exists only in theory (2) is a non-contacting magnetic sensor (3) can operate only a few times before failure (4) produces very large voltages</p>
80.	<p>For turbulent flow, the velocity at the center is _____ times the mean velocity.</p> <p>(1) 1.2 (2) 2.2 (3) 2 (4) 3.333</p>
81.	<p>Typical range of thyristor turn OFF time is</p> <p>(1) $3 - 10 \mu\text{s}$ (2) $3 - 50 \mu\text{s}$ (3) $3 - 100 \mu\text{s}$ (4) $3 - 500 \mu\text{s}$</p>

Question No.	Questions
82.	<p>String efficiency depends upon</p> <ul style="list-style-type: none">(1) voltage rating of whole string(2) no. of SCR in the string(3) voltage rating of one SCR(4) all of these
83.	<p>A thyristor string is made of a no. of SCR connected in series and parallel. The string have voltage and current of 11 KV and 4 KA. The voltage and current rating of available SCRs are 1800 V and 1000 A. For a string efficiency of 90% let the number of SCRs in series and parallel are a and b respectively. Then the value of a and b will be</p> <ul style="list-style-type: none">(1) 5, 7(2) 4, 6(3) 7, 5(4) 6, 4
84.	<p>A 200 A thyristor is to be operated in parallel with a 300 A thyristor. The ON state voltage drops are 1.5 V and 1.2 Volts. What is the value of resistance R to be connected in series with each thyristor, so that current through the combination is 500 A and each of them is fully loaded ?</p> <ul style="list-style-type: none">(1) $0.03 \times 10^{-2} \Omega$(2) $0.3 \times 10^{-3} \Omega$(3) $3.0 \times 10^{-3} \Omega$(4) $0.3 \times 10^{-2} \Omega$

Question No.	Questions
92.	<p>If peak value of phase mmf is F_{\max}, then peak value of the rotating field caused by three phase is</p> <p>(1) $(3/2) F_{\max}$ (2) F_{\max} (3) $3 F_{\max}$ (4) $(1/2) F_{\max}$</p>
93.	<p>A 50 Hz, 4 pole turbo generator rated at 20 MVA, 13.2 KV has inertia constant $H = 3 \text{ kW sec / KVA}$. The kinetic energy stored in the rotor is</p> <p>(1) 80 MJ (2) 60 MJ (3) 20 MJ (4) 10 MJ</p>
94.	<p>An alternator is supplying a load of 300 kW of a p.f. of 0.6 lagging. If the power factor is raised to unity. How many more kilowatts can alternator supply for the same KVA loading</p> <p>(1) 100 kW (2) 200 kW (3) 300 kW (4) 500 kW</p>
95.	<p>A 300 kVA, single phase transformer is designed to have resistance of 1.5 % and max. efficiency occurs at load of 173.2 kVA. When supplying the full load at 0.8 p.f. lagging at normal voltage, the efficiency will be</p> <p>(1) 12.6% (2) 97.6% (3) 35.5% (4) 29.6%</p>
96.	<p>For constant load current at which power factor the efficiency of a transformer will be maximum ?</p> <p>(1) Zero power factor (2) Unity power factor (3) Leading power factor (4) Lagging power factor</p>

Question No.	Questions
97.	<p>The all-day efficiency is the term related to</p> <ol style="list-style-type: none"> (1) Power transformer (2) Distribution transformer (3) Current transformer (4) Voltage transformer
98.	<p>Satisfactory commutation of DC machine requires</p> <ol style="list-style-type: none"> (1) Smooth, concentric commutator properly undercut (2) Brushes should smoothly run in the holders (3) Brushes should be of proper grade and size (4) All of the above
99.	<p>In a 3 - Φ induction motor running at full load which of these parameters is stationary with respect to the stator mmf wave ?</p> <ol style="list-style-type: none"> (1) Stator winding (2) Rotor winding (3) Both rotor and stator winding (4) Rotor mmf wave
100.	<p>The damper windings also called the squirrel cage winging's damper grids</p> <ol style="list-style-type: none"> (1) consists of short-circuited copper bars embedded in the field pole faces (2) are provided in a synchronous motor to make itself starting (3) are provided on the stator for improving power factor (4) both (1) and (2)

(Set-“X”)

(DO NOT OPEN THIS QUESTION BOOKLET BEFORE TIME OR UNTIL YOU ARE ASKED TO DO SO)

(M.Phil/Ph.D/URS-EE-2018)

Code

D

Subject : ELECTRICAL ENGG.

Sr. No. 100004


INSTRUCTIONS BEFORE START

1. All questions are compulsory.
2. The candidates must return the Question-answer-sheet to the Invigilator concerned ~~before leaving the Examination Hall,~~ failing which a case of use of unfair-means / mis-behaviour will be registered against him / her, in addition to lodging of an FIR with the police. Further the answer-sheet of such a candidate will not be evaluated.
3. Keeping in view the transparency of the examination system, carbonless OMR Sheet is provided to the candidate so that a copy of OMR Sheet may be kept by the candidate.
4. Question Booklet along with answer key of all the A, B, C, D code will be got uploaded on the University website after the conduct of Entrance Examination. In case there is any discrepancy in the Question Booklet / Answer Key, the same may be brought to the notice of the Controller of Examination in writing / through E.Mail within 24 hours of uploading the same on the University Website. Thereafter, no complaint in any case, will be considered
5. The candidate **MUST NOT** do any rough work or writing in the OMR Answer-Sheet. Rough work, if any, may be done in the question book-let itself. Answers **MUST NOT** be ticked in the Question book-let.
6. **There will be no Negative marking. Each correct answer will be awarded one full mark. Cutting, erasing, overwriting and more than one answer in OMR Answer-Sheet will be treated as incorrect answer.**
7. Use only Black or Blue **BALL POINT PEN** of good quality in the OMR Answer-Sheet.
8. **BEFORE ANSWERING THE QUESTIONS, THE CANDIDATES SHOULD ENSURE THAT THEY HAVE BEEN SUPPLIED CORRECT AND COMPLETE BOOK-LET. COMPLAINTS, IF ANY, REGARDING MISPRINTING ETC. WILL NOT BE ENTERTAINED 30 MINUTES AFTER STARTING OF THE EXAMINATION.**




Question No.	Questions
1.	<p>Typical range of thyristor turn OFF time is</p> <p>(1) 3 – 10 μs</p> <p>(2) 3 – 50 μs</p> <p>(3) 3 – 100 μs</p> <p>(4) 3 – 500 μs</p>
2.	<p>String efficiency depends upon</p> <p>(1) voltage rating of whole string</p> <p>(2) no. of SCR in the string</p> <p>(3) voltage rating of one SCR</p> <p>(4) all of these</p>
3.	<p>A thyristor string is made of a no. of SCR connected in series and parallel. The string have voltage and current of 11 KV and 4 KA. The voltage and current rating of available SCRs are 1800 V and 1000 A. For a string efficiency of 90% let the number of SCRs in series and parallel are a and b respectively. Then the value of a and b will be</p> <p>(1) 5, 7</p> <p>(2) 4, 6</p> <p>(3) 7, 5</p> <p>(4) 6, 4</p>

Question No.	Questions
4.	<p>A 200 A thyristor is to be operated in parallel with a 300 A thyristor. The ON state voltage drops are 1.5 V and 1.2 Volts. What is the value of resistance R to be connected in series with each thyristor, so that current through the combination is 500 A and each of them is fully loaded ?</p> <p>(1) $0.03 \times 10^{-2} \Omega$ (2) $0.3 \times 10^{-3} \Omega$ (3) $3.0 \times 10^{-3} \Omega$ (4) $0.3 \times 10^{-2} \Omega$</p>
5.	<p>If a latching current for the circuit shown in figure is 2 mA. Obtain the value of minimum width of the property turn ON the SCR ?</p> <div data-bbox="352 898 935 1182" style="text-align: center;"> <p style="text-align: center;">$I_L = 2 \text{ mA}$</p> </div> <p>(1) $3 \mu\text{s}$ (2) $3.1 \mu\text{s}$ (3) $3.2 \mu\text{s}$ (4) $3.3 \mu\text{s}$</p>
6.	<p>A thyristor will be triggered when $V_g = 1.5$ volt and $I_g = 100$ mA in the given figure. Calculate the value of R in ohm is</p> <div data-bbox="288 1480 959 1854" style="text-align: center;"> </div> <p>(1) 65 (2) 3.714 (3) 37.14 (4) 60</p>

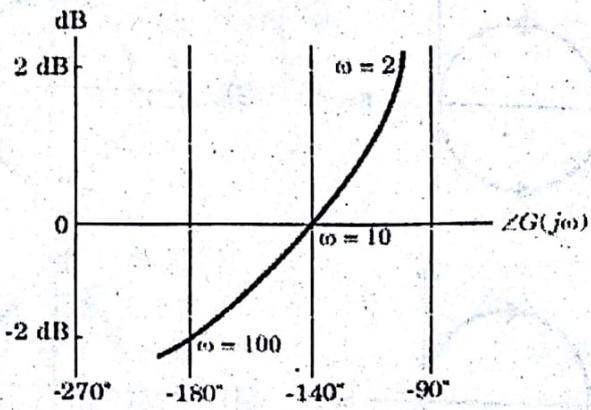Question No.	Questions
7.	The peak to peak source current ripple in amperes is (1) 0.96 (2) 0.144 (3) 0.192 (4) 0.288
8.	The average source current in amperes in steady state is (1) 3/2 (2) 5/3 (3) 5/2 (4) 15/4
9.	The rms value of load phase voltage is (1) 105.1 V (2) 141.4 V (3) 212.2 V (4) 282.8 V
10.	In the DC bus voltage $V_d = 300$ V, the power consumed by three phase load is (1) 1.5 kW (2) 2.0 kW (3) 2.5 kW (4) 3.0 kW
11.	Consider the gain-phase plot shown in fig. The gain margin and phase margin are <div style="text-align: center;">  <p>The figure shows a Bode plot for the transfer function ZG(jω). The vertical axis represents gain in dB, with markings at -2 dB, 0 dB, and 2 dB. The horizontal axis represents phase in degrees, with markings at -270°, -180°, -140°, and -90°. The plot shows a curve that starts at approximately -2 dB at -180° and rises to 2 dB at -90°. Key points on the curve are labeled with frequencies: ω = 100 at -180°, ω = 10 at -140°, and ω = 2 at -90°. The curve crosses the 0 dB line at a phase of -140°.</p> </div> Fig (1) -2 dB, 40° (2) 2 dB, 40° (3) 2 dB, 140° (4) -2 dB, 140°

Question No.	Questions
12.	The root locus of a unity feed function is given by (1) $k/s (s + 1) (s + 2)$ (2) $k (s + 1)/s (s + 2)$ (3) $k (s + 2)/s (s + 1)$ (4) $ks/(s + 1) (s + 2)$
13.	The transfer function $\frac{1+0.5s}{1+s}$ represents (1) Lag network (2) Lead network (3) Lag-lead Network (4) Proportional controller
14.	If the stability error for a step input and speed of the response be the criteria for design, the suitable controller will be (1) P Controller (2) PI Controller (3) PD Controller (4) PID Controller
15.	The open loop transfer function of a feedback system is $G(s) H(s) = \frac{K(s+1)}{(1-s)}$ The nyquist plot of this system is <div style="display: flex; flex-wrap: wrap; justify-content: space-around;"> <div style="text-align: center;"> <p>(1)</p> </div> <div style="text-align: center;"> <p>(2)</p> </div> <div style="text-align: center;"> <p>(3)</p> </div> <div style="text-align: center;"> <p>(4)</p> </div> </div>

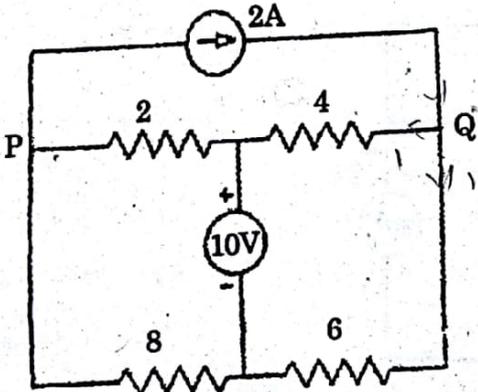
Question No.	Questions
16.	<p>The equation for 25 cycles electric current sine wave having rms value of 30 amps, will be</p> <p>(1) $42.4 \sin 50\pi t$ (2) $30 \sin 50\pi t$</p> <p>(3) $30 \sin 25\pi t$ (4) $42.4 \sin 25\pi t$</p>
17.	<p>The equation of an emf is given by $e = I_m \left[\sqrt{(R^2 + 4\omega^2 L^2)} \right] \sin 2\omega t$. The amplitude of the wave will be</p> <p>(1) $I_m \left[(R^2 + 4\omega^2 L^2)^{1/2} \right]$ (2) $\sqrt{2} I_m \left[(R^2 + 4\omega^2 L^2)^{1/2} \right]$</p> <p>(3) $\left[I_m (R^2 + 4\omega^2 L^2) \right]^{1/2}$ (4) $2 I_m \left[(R^2 + 4\omega^2 L^2)^{1/2} \right]$</p>
18.	<p>In the figure, the potential difference between points P and Q is</p>  <p>(1) 6 (2) -6</p> <p>(3) 10 (4) 12</p>

Question No.

Questions

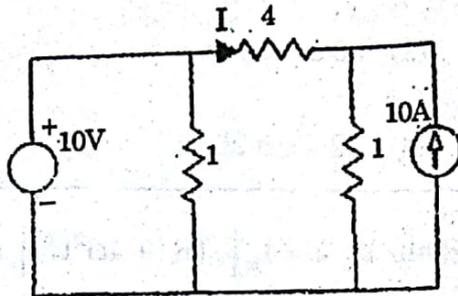19.


In the network shown, what is the electric current I in the direction shown



- (1) 0 A.
 (2) $1/3$ A.
 (3) $5/6$ A.
 (4) 4 A.

20.

In the figure given, the value of R is

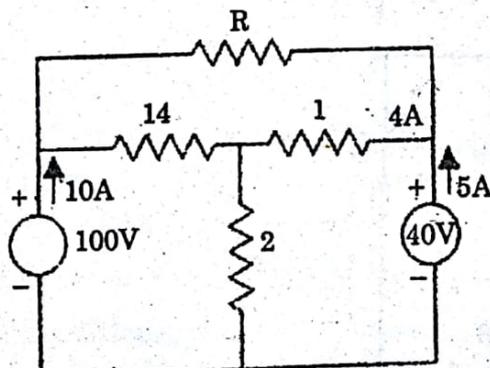


- (1) 10Ω
 (2) 12Ω
 (3) 18Ω
 (4) 24Ω

Question No.	Questions
25.	<p>A power station supplies the peak load of 50 MW, 40 MW and 70 MW to three localities. The annual load factor is 0.50 p.u. and the diversity factor of the load at the station is 1.55 the maximum demand on the station and average load respectively will be</p> <p>(1) 51.61 MW (2) 57.5 MW (3) 53 MW (4) 52 MW</p>
26.	<p>Which of the following circuit breakers produce least arc energy ?</p> <p>(1) Air blast (2) Air break (3) Minimum oil (4) Plain oil</p>
27.	<p>A 100 Km long transmission line is loaded at 110 kV. If the loss of line is 5 MW and the load is 150 VA the resistance of the line is</p> <p>(1) 4.65 ohms / phase (2) 2.26 ohms / phase (3) 8.06 ohms / phase (4) 6.06 ohms / phase</p>
28.	<p>A three-phase, 33 kV oil circuit breaker is rated 1200 A, 2000 MVA, 3 s. The symmetrical breaking current is</p> <p>(1) 1200 A (2) 3600 A (3) 35 kA (4) 104.8 kA</p>
29.	<p>A 3 core cable gives on test a capacitance of 3.7 microfarad between two cores. Find the line charging current of the cable when it is connected to 11 kV, 50 Hz system ?</p> <p>(1) 14.76 A (2) 1.476 A (3) 14.7 mA (4) 1 A</p>


Question No.	Questions
30.	<p>The most suitable circuit breaker for short line fault without switching resistor is</p> <p>(1) Oil circuit breaker (2) Air blast circuit breaker (3) SF₆ breaker (4) None of these</p>
31.	<p>The hexadecimal equivalent of the octal number 171.62 is</p> <p>(1) 3C1.C0 (2) 79.C8 (3) 89.C7 (4) 97.8C</p>
32.	<p>Which of the following circuit can be used as parallel to series converter ?</p> <p>(1) Digital Counter (2) Decoder (3) De-multiplexer (4) Multiplexer</p>
33.	<p>How many flip-flops are required to construct a decade counter ?</p> <p>(1) 10 (2) 3 (3) 4 (4) 2</p>
34.	<p>Which is not a type of ROM ?</p> <p>(1) Mask ROM (2) PROM (3) EEPROM (4) XROM</p>
35.	<p>A stage in shift register consist of</p> <p>(1) Latch (2) Flip flop (3) Byte of storage (4) four bits of storage</p>


Question No.	Questions
36.	The closed loop transfer function of a system is $T(s) = \frac{(s+8)(s+6)}{s^5 + s^4 + 4s^3 - 4s^2 + 3s - 2}$ The number of poles in RHP and LHP are (1) 4,1 (2) 1,4 (3) 3,2 (4) 2,3
37.	For a second order system settling time $T_s = 7$ sec and peak time $T_p = 3$ sec. The location of poles are (1) $-0.97 \pm j 0.69$ (2) $-0.69 \pm j 0.97$ (3) $-1.047 \pm j 0.571$ (4) $-0.571 \pm j 1.047$
38.	The open loop transfer function of a unity feedback system is $G(s) = \frac{50}{(1+0.1s)(1+2s)}$ The position, velocity and acceleration error constants are respectively (1) 0, 0, 250 (2) 50, 0, 0 (3) 0, 250, ∞ (4) ∞ , 50, 0 <i>Handwritten notes:</i> $\frac{1}{1+0.1s+1+s}$ $\frac{1}{1+s}$ $\frac{50}{1+s}$ $\frac{50}{1+s}$ $50, 0$
39.	A unity feedback system has a forward path transfer function is $G(s) = \frac{10(1+4s)}{s^2(1+s)}$ If the system is subjected to an input $r(t) = 1 + t + \frac{t^2}{2}, t > 0$ the steady state error of the system will be (1) 1 (2) 0.1 (3) 10 (4) ∞

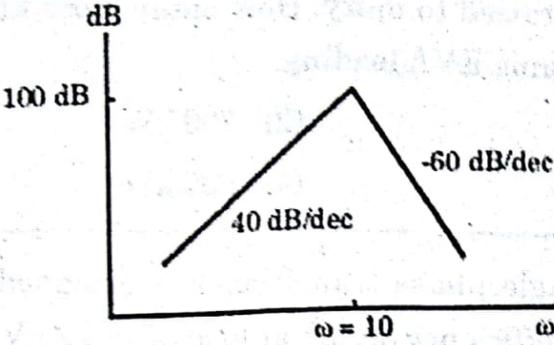Question No.	Questions
40.	<p>For the Bode plot shown in figure, the transfer function is</p>  <p>(1) $\frac{100 s^2}{(1+0.1s)^3}$ (2) $\frac{1000 s^2}{(1+0.1s)^6}$</p> <p>(3) $\frac{15.6 s^2}{(1+0.1s)^6}$ (4) None</p>
41.	<p>A rotating electrical machine having its self-inductance's of both the stator and the rotor windings independent of the rotor position will definitely not develop</p> <p>(1) Starting Torque (2) Synchronizing torque</p> <p>(3) Hysteresis Torque (4) Reluctance torque</p>
42.	<p>If peak value of phase mmf is F_{max}, then peak value of the rotating field caused by three phase is</p> <p>(1) $(3/2) F_{max}$ (2) F_{max}</p> <p>(3) $3 F_{max}$ (4) $(1/2) F_{max}$</p>
43.	<p>A 50 Hz, 4 pole turbo generator rated at 20 MVA, 13.2 KV has inertia constant $H = 3$ kW sec / KVA. The kinetic energy stored in the rotor is</p> <p>(1) 80 MJ (2) 60 MJ</p> <p>(3) 20 MJ (4) 10 MJ</p>

Question No.	Questions
48.	Satisfactory commutation of DC machine requires (1) Smooth, concentric commutator properly undercut (2) Brushes should smoothly run in the holders (3) Brushes should be of proper grade and size (4) All of the above
49.	In a 3- ϕ induction motor running at full load which of these parameters is stationary with respect to the stator mmf wave ? (1) Stator winding (2) Rotor winding (3) Both rotor and stator winding (4) Rotor mmf wave
50.	The damper windings also called the squirrel cage winging's damper grids (1) consists of short-circuited copper bars embedded in the field pole faces (2) are provided in a synchronous motor to make itself starting (3) are provided on the stator for improving power factor (4) both (1) and (2)
51.	Mho relay is used for the protection of (1) medium length lines (2) long transmission lines (3) short length lines (4) no length criterion

Question No.	Questions
56.	<p>A single phase one pulse controlled circuit has a resistance R and counter emf E load $400 \sin(314t)$ as the source voltage. For a load counter emf of 200 V, the range of firing angle control is</p> <p>(1) 30° to 150° (2) 30° to 180° (3) 60° to 120° (4) 60° to 180°</p>
57.	<p>Let of a thyristor V_{c1}, V_{c2}, V_{c3} are forward break over voltage for gate current I_{g1}, I_{g2}, I_{g3} respectively. Then</p> <p>(1) $V_{c1} > V_{c2} > V_{c3}$ when $I_{g1} > I_{g2} > I_{g3}$. (2) $V_{c1} > V_{c2} > V_{c3}$ when $I_{g1} < I_{g2} < I_{g3}$ (3) $V_{c1} = V_{c2} = V_{c3}$ any value of I_g. (4) $V_{c1} > V_{c2} > V_{c3}$ when $I_{g1} \geq I_{g2} \geq I_{g3}$</p>
58.	<p>Triacs cannot be used in AC voltage regulator for a</p> <p>(1) Resistive load (2) Inductive load (3) Back emf load (4) Resistive Inductive</p>
59.	<p>Latching current for an SCR inserted between a dc voltage source of 200 V and load is 100 mA. Compute the minimum rate of width pulse required to turn ON the SCR in case load consists of $R = 20 \Omega$ in series with $L = 0.2$ H</p> <p>(1) $200 \mu s$ (2) $300 \mu s$ (3) $150 \mu s$ (4) $100 \mu s$</p>

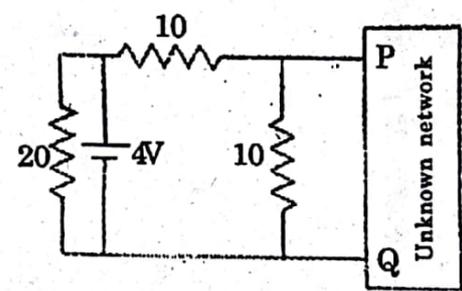Question No.	Questions
60.	<p>Delay time is defined by the interval when</p> <p>(1) gate current increases from 90% to 100% of its final value (2) anode current reaches 10% from forward leakage current (3) anode voltage drops from 100% to 90% of its actual value (4) all of these</p>
61.	<p>In the given figure, the Thevenin equivalent voltage and impedance as seen from the terminals P-Q is given by</p>  <p>(1) 4 V and 7.5 Ω (2) 2 V and 7.5 Ω (3) 4 V and 5 Ω (4) 2 V and 5 Ω</p>
62.	<p>A coil having a resistance of 5 Ω and inductance of 0.1 H is connected in series with a condenser of capacitance 50 μF. A constant alternating voltage of 200 V is applied to the circuit. The voltage across coil at resonance is</p> <p>(1) 200 V (2) 1788 V (3) 1800 V (4) 2000 V</p>
63.	<p>An RLC series circuit resonates at a frequency ω_r, the ratio of $\omega_r L/R = 10$ the variable frequency voltage applied to the circuit is $20 \sin(\omega t + \pi/3)$ the voltage measured across the capacitance</p> <p>(1) $200/\sqrt{2}$ (2) $220/\sqrt{2}$ (3) $20/\sqrt{2}$ (4) $1/2$</p>

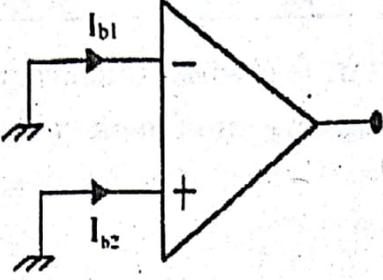Question No.	Questions
68.	<p>For the op-amp shown in the figure, the bias currents are $I_{b1} = 450 \text{ nA}$ and $I_{b2} = 350 \text{ nA}$. The values of the input bias current (I_b) and the input offset current (I_f) are</p>  <p>(1) $I_b = 800 \text{ nA}$, $I_f = 50 \text{ nA}$ (2) $I_b = 800 \text{ nA}$, $I_f = 100 \text{ nA}$ (3) $I_b = 400 \text{ nA}$, $I_f = 50 \text{ nA}$ (4) $I_b = 400 \text{ nA}$, $I_f = 100 \text{ nA}$</p>
69.	<p>A Hall Effect sensor</p> <p>(1) exists only in theory (2) is a non-contacting magnetic sensor (3) can operate only a few times before failure (4) produces very large voltages</p>
70.	<p>For turbulent flow, the velocity at the center is _____ times the mean velocity.</p> <p>(1) 1.2 (2) 2.2 (3) 2 (4) 3.333</p>
71.	<p>A psychrometric chart is used to determine</p> <p>(1) pH (2) Sound velocity in glasses (3) CO_2 concentration (4) Relative humidity</p>

Question No.	Questions
72.	<p>The dynamic characteristics of capacitive transducer are similar to those of</p> <p>(1) low pass filter (2) high pass filter (3) notch filter (4) band stop filter</p>
73.	<p>The effect of error damping is to</p> <p>(1) provide larger settling time (2) delay the response (3) reduce steady state error (4) any of the above</p>
74.	<p>The bridge method commonly used for finding mutual inductance is</p> <p>(1) Heaviside Campbell bridge (2) Schering bridge (3) De Sauty's bridge (4) Wien bridge</p>
75.	<p>The bridge circuit shown in the figure below is used for the measurement of an unknown element Z_x. The bridge circuit is best suited when Z_x is a</p> <div data-bbox="319 1388 845 1702" data-label="Diagram"> </div> <p>(1) Lossy capacitor (2) Low Q inductor (3) High resistance (4) Low resistance</p>

Question No.	Questions
84.	<p>If $\delta(t)$ denotes a unit impulse then Laplace Transform of $\frac{d^2 \delta(t)}{dt^2}$ will be</p> <p>(1) l (2) s^2 (3) s (4) s^{-2}</p>
85.	<p>The state equation of LTI system is represented by</p> $\dot{x} = \begin{bmatrix} 0 & 0 \\ -2 & -1 \end{bmatrix} x + \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} u$ <p>The Eigen values are</p> <p>(1) $-1, +1$ (2) $0.5 \pm j 1.323$ (3) $-1, -1$ (4) None</p>
86.	<p>Line integral can be transformed into a surface integral by using</p> <p>(1) Divergence theorem (2) Gauss theorem (3) Stokes theorem (4) None of these</p>
87.	<p>Four fundamental equations of electromagnetics are known as</p> <p>(1) Fleming's laws (2) Faraday's laws (3) Lorentz equations (4) Maxwell's equations</p>
88.	<p>For a linear electromagnetic circuit, which of the following statements is true ?</p> <p>(1) Field energy is equal to the co-energy (2) Field energy is greater than the co-energy (3) Field energy is lesser than the co-energy (4) Co-energy is zero</p>

Question No.	Questions
93.	<p>A conductor of length L has current I passing through it, when it is placed parallel to strong magnetic field. The force experienced by the conductor will be</p> <p>(1) BIL (2) BI^2L (3) BI^2L (4) Zero</p>
94.	<p>Cork Screw rule is used to find</p> <p>(1) Direction of magnetic field (2) Direction of electric field (3) Direction of current (4) Direction of emf</p>
95.	<p>A point pole has a strength of $4\pi \times 10^{-4}$ weber. The force in Newtons on a point pole of $4\pi \times 1.5 \times 10^{-4}$ weber placed at a distance of 10 cm from it will be</p> <p>(1) 20N (2) 15N (3) 7.5N (4) 3.75N</p>
96.	<p>In a sample it is observed that a carrier takes $100\mu s$ to over a distance of 10 cm. If the applied external field is 10^4 V/cm; find the mobility</p> <p>(1) $10^7 \text{ cm}^2/\text{Vs}$ (2) $10^{-3} \text{ cm}^2/\text{Vs}$ (3) $10 \text{ cm}^2/\text{Vs}$ (4) $10^7 \text{ m}^2/\text{Vs}$</p>
97.	<p>The current gain of a bipolar transistor drops at high frequency because of</p> <p>(1) Transistor internal capacitances (2) High current effects in the base (3) Parasitic inductive elements (4) The Early effect</p>

M. Phil/ Phd/URS Entrance Examination Answer Key

Sr. No.	Set-A	Set-B	Set-C	Set-D
1	B	D	B	C
2	D	C	D	D
3	A	A	C	C
4	B	A	D	D
5	B	D	A	D
6	C	C	C	D
7	D	C	D	C
8	A	D	B	B
9	D	B	B	B
10	D	A	D	D
11	A	D	D	A
12	A	B	D	A
13	D	C	A	A
14	C	C	A	D
15	B	A	D	D
16	C	A	B	A
17	A	C	D	A
18	B	C	B	B
19	D	A	D	A
20	A	C	C	B
21	B	C	B	D
22	D	D	A	B
23	C	C	A	C
24	D	D	C	C
25	A	D	B	A
26	C	D	A	A
27	D	C	B	C
28	B	B	C	C
29	B	B	D	A
30	D	D	D	C
31	A	B	D	B
32	A	D	B	D
33	A	A	C	C
34	D	B	C	D
35	D	B	A	A
36	A	C	A	C
37	A	D	C	D
38	B	A	C	B
39	A	D	A	B
40	B	D	C	D
41	D	D	B	D
42	C	D	D	A
43	A	A	A	B
44	A	A	B	B
45	D	D	B	B
46	C	B	C	B
47	C	D	D	B

ml
17-11-19

SA
17/11/18

SA
17/11/18

SA

Electrical Engg.

Sr. No	Set-A	Set-B	Set-C	Set-D
48	D	B	A	D
49	B	D	D	D
50	A	C	D	D
51	D	D	A	B
52	D	A	A	A
53	A	B	A	A
54	A	B	D	C
55	D	B	D	B
56	B	B	A	A
57	D	B	A	B
58	B	D	B	C
59	D	D	A	D
60	C	D	B	D
61	D	B	A	D
62	A	D	A	C
63	B	C	D	A
64	B	D	C	A
65	B	A	B	D
66	B	C	C	C
67	B	D	A	C
68	D	B	B	D
69	D	B	D	B
70	D	D	A	A
71	D	A	D	D
72	B	A	C	D
73	C	D	A	A
74	C	C	A	A
75	A	B	D	D
76	A	C	C	B
77	C	A	C	D
78	C	B	D	B
79	A	D	B	D
80	C	A	A	C
81	B	B	C	B
82	A	A	D	D
83	A	A	C	A
84	C	C	D	B
85	B	B	D	B
86	A	A	D	C
87	B	B	C	D
88	C	C	B	A
89	D	D	B	D
90	D	D	D	D
91	C	A	D	A
92	D	A	A	A
93	C	A	B	D
94	D	D	B	C
95	D	D	B	B
96	D	A	B	C
97	C	A	B	A
98	B	B	D	B
99	B	A	D	D
100	D	B	D	A

m h
17-11-18

Pa
17/11/18

17/11/18

all